

## Number Systems & Codes

⇒ Decimal number system.

(b) base = 10

(i-i) no. of digits → 0, 1, 2, 3, 4, 5, 6, 7, 8, 9

$$\# (\underbrace{\text{no. of digits}}_k \cdot \underbrace{\text{no. of digits}}_l) \rightarrow (345.12)_{10}$$

$$(a_{k-1} \dots a_1 a_0 a_{-1}) \cdot (a_{-1} a_{-2} \dots a_{-p})$$

$$N_b = a_{k-1} b^{k-1} + a_{k-2} b^{k-2} + \dots + a_0 b^0 + a_{-1} b^{-1} + a_{-2} b^{-2} + \dots + a_{-p} b^{-p}$$

$$= \sum_{i=-p}^{k-1} a_i b^i$$

$$a < b - 1$$

	b
Decimal	10
Binary	2
Octal	$2^3$
Hexadecimal	16

$$0, 1, \dots, 9, A, B, C, D, E, F$$

$$(00) (01) (02) (03) (04) (05)$$

$$\# N_b = a_{k-1} b^{k-1} + a_{k-2} b^{k-2} + \dots + a_0 b^0$$

$$\frac{N_b}{b_2} = \frac{a_{k-1} b_2^{k-1} + a_{k-2} b_2^{k-2} + \dots + a_0 b_2^0 + \left( \frac{a_0}{b_2} \right)}{b_2}$$

$$\frac{N_b}{b_2} = a_0 + \overset{\curvearrowleft}{a_0}$$

$$\frac{a_0}{b_2} = a_1 + \overset{\curvearrowleft}{a_1}$$

$$\text{Ex. } 34.12_{10}$$

$$100010.00011_2$$

$$N_b \times b_2 = a_{-1} + \underbrace{a_{-2} b_2^{-1} + a_{-3} b_2^{-2} + \dots + a_{-p} b_2^{-p}}_{N_b'}$$

$$N_b' \times b_2 = a_{-2} + \dots + \underbrace{a_{-p} b_2^{-p}}_{\text{---}} \quad \underline{b_2 > b_{-1}} \quad \underline{(10 \rightarrow 2)}$$

Decimal	Binary	$w_4$	$w_3$	$w_2$	$w_1$
0	0000	8	4	2	1
1	0001				
2	0010				
3	0011				
4	0100				
5	0101				
6	0110				
7	0111				
8	1000				
9	1001				

for  
binary  
to  
decimal

$$\left\{ \begin{array}{l} N = w_4x_4 + w_3x_3 + w_2x_2 + w_1x_1 \\ (x_4 x_3 x_2 x_1) \\ 8 \quad 4 \quad 2 \quad 1 \\ \therefore N = 8x_4 + 4x_3 + 2x_2 + x_1 \end{array} \right.$$

$$x_i - 0/1$$

# Binary to octal

$$\begin{array}{cccc|cc} 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ & & & & & & \\ & 1 & & 1 & & 3 & 5 \end{array} \rightarrow (1135)_8$$

(For octal :

$$x_4 x_3 x_2 x_1 \\ 8^3 8^2 8^1 8^0$$

$$N = 8^3 x_4 + 8^2 x_3 + 8 x_2 + 1 x_1$$

$$x_i \rightarrow 0, 1, 2, 3, \dots, 7$$

# Binary to Hexa:

$$\begin{array}{cccc|cc} 0 & 0 & 1 & 0 & 1 & 0 & 1 \\ & 2 & & 5 & & 4 & \\ & & & & & & \end{array} \rightarrow (25D)_{16}$$

# Weighted code:

8421-code  $\rightarrow$  Binary coded decimal code

$$N_{10} = w_4x_4 + w_3x_3 + w_2x_2 + w_1x_1$$

Ex: wt 2421

Decimal	2421 code
0	0000
1	0001
2	0010 / 1000
3	0011 / 1001
4	0100 / 1010
5	1011 / 0101
6	1100 / 0110
7	0111 / 1101
8	1110
9	1111

wt  $\rightarrow$  642 -3

Ex:

0	0000
1	0101
2	0010
3	1001

(Non-weighted code)

#	Decimal	Excess-3	(+3)
0		0011	
1		0100	
2		0101	
3		0110	
4		0111	
5		1000	
6		1001	
7		1010	
8		1011	
9		1100	

# Cyclic code: Two codes differ in one digit.

Gray code: One popular cyclic code

1bit gray code	1G	2G	3 bit gray code	n bit Gray code
			000 001 011 010 111 110 101 100	0000 0001 0011 0010 0111 0110 0101 0100
0	0	00	000	0000 0001 0011 0010 0111 0110 0101 0100
1	1	01	001	
		10	011	
		11	010	

$A$	$B$	$C_n = B_n$
0	000	000
1	001	001
2	011	010
3	010	011
4	110	100
5	111	101
6	101	110


$n$  bit binary is  $n$ -bit

$$C_1 = B_1 \\ C_2 = B_2 \oplus B_1 \\ C_3 = B_3 \oplus B_2 + B_1$$


XOR

00	-0
11	-0
01	-1
10	-1

$b_3 b_2 b_1 b_0 = B$

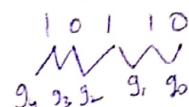

## # SWITCHING ALGEBRA :-

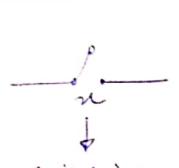

Switching Variable

open  
closed

$$\begin{array}{c} A \xrightarrow{x} \xrightarrow{y} B \\ \text{serial connection} \end{array} = \underline{x \cdot y} \quad (\wedge, \Lambda, \text{AND}) \quad \rightarrow \text{Product}$$

$$x=0; \text{ if } x \neq 1 \\ x=1; \text{ if } x \neq 0$$

$$\begin{array}{c} A \xrightarrow{x} \xrightarrow{y} B \\ \text{parallel connection} \end{array} = \underline{x+y} \quad (\vee, \cup, \text{OR}) \quad \rightarrow \text{Sum}$$

$$x' \rightarrow \text{NOT}$$

0	1
1	0

$$\rightarrow x_1, x_2, \dots, x_n = \{0, 1\}, +, \cdot, ', \wedge, \vee$$

$$\# \{0, 1\} \quad \{+, \cdot, ', \wedge, \vee\}$$

Basic properties:

(1) Idempotency :-

$$x + x = x \\ x \cdot x = x$$

} Useful to minimize

Proof: Induction (Take all values)

$$\begin{array}{ll} 1+1=1 & 1 \cdot 1=1 \\ 0+0=0 & 0 \cdot 0=0 \end{array}$$

(2) Commutative :-

$$x+y = y+x$$

$$x \cdot y = y \cdot x$$

Proof:  
same

(3) Associative :-

$$x+(y+z) = (x+y)+z$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

(4) Distributive :-

Note:  $5 \times (7+3) = 5 \times 7 + 5 \times 3$

$$5 + (7 \times 3) \neq (5+7) \times (5+3)$$

→ Multiplication / Product is distributive over sum (+),  
(+)

but (+) is not distributive over (-)

In NORMAL ALGEBRA

→ In switching Algebra:

(+) distributes over (-)

& (-) distributes over (+)

$$\begin{aligned} x + y \cdot z &= (x+y) \cdot (x+z) \\ x \cdot (y+z) &= (x \cdot y) + (x \cdot z) \end{aligned} \quad ] \text{DISTRIBUTIVE}$$

# Simplification rules :-

$$x+1 = 1$$

$$x+0 = x$$

$$x \cdot 1 = x$$

$$x \cdot 0 = 0$$

\* (1) Absorption :-

$$x + x \cdot y = x$$

$$x \cdot (x+y) = x$$

} same result on exchanging  
(-) & (+),  
duality property  
of Boolean Algebra

Proof:-

$$\begin{aligned} ① x + x \cdot y &= x(1+y) \\ &= x \end{aligned}$$

$$\begin{aligned} ② x \cdot x + x \cdot y &= x + x \cdot y \\ &= x \end{aligned}$$

## Absorption (contd)

$$x + x' = 1$$

$$x \cdot x' = 0$$

(2) Consensus:- (V. Imp)

$$\begin{aligned} x \cdot y + x' \cdot z + y \cdot z &= x \cdot y + x' \cdot y \\ \text{&} \quad (x+y) \cdot (x'+z) \cdot (y+z) &= (x+y) \cdot (x'+y) \end{aligned} \quad (Z \rightarrow Z)$$

By  
duality

Proof:

$$\begin{aligned} ① \quad x \cdot y + x' \cdot z + y \cdot z &= x \cdot y + x' \cdot z + y \cdot z \cdot (x+x') \\ &= x \cdot y + x' \cdot z + y \cdot z \cdot x + y \cdot z \cdot x' \\ &= x \cdot (y + y \cdot z) + x' \cdot (z + y \cdot z) \\ &= x \cdot y + x' \cdot z \end{aligned}$$

$$\begin{aligned} ② \quad (x+y) \cdot (x'+z) \cdot (y+z) &= (x+y) \cdot (x'+z) \cdot (y+z + \cancel{x \cdot x'}) \\ &= (x+y) \cdot (x'+z) \cdot (y+z+x) \cdot (y+z+x') \\ &\cancel{\text{EXPANDING}} \\ &= (\underline{x+y}) \cdot (\underline{x+y+z}) \cdot (\underline{x'+z}) \cdot (\underline{y+z+x}) \quad [A - (A+B) = A] \\ &= (x+y) \cdot (x'+z) \end{aligned}$$

# If  $f_1$  &  $f_2$  are 2 switching expressions :-

$$f_2, f_1 = \{x_1, x_2, x_3, \dots, x_n, +, \circ, '\}$$

$f_1 = 0/1 \xrightarrow{\text{Truth values}}$   $f_2 = 0/1 \quad | \rightarrow f_1, f_2 \text{ can be}$   
switching variables

$$f_1 \cdot f_2, f_1 + f_2, f_1', f_2'$$

↳ All switching expression.

Switching expression:  $f(x_1, x_2, x_3, \dots, x_n)$   
function

x	y	z	f
0	0	0	$x'y'z'$
0	0	1	$x'y'z$
0	1	0	$x'y'z'$
0	1	1	$x'yz$
1	0	0	$xy'z'$
1	0	1	$xy'z$
1	1	0	$xyz'$
1	1	1	$xyz$

$$\begin{array}{r} 0-x \\ \underline{1-x} \end{array}$$

Now say we have:

x	y	z	f	What is f?
0	0	0	1 ✓	
0	0	1	0	$f = x'y'z' + xy'z' + xyz$
0	1	0	0	
0	1	1	0	
1	0	0	1 ✓	$\therefore f$ is not unique
1	0	1	0	
1	1	0	0	
1	1	1	1 ✓	

Now  $f = x'y'z' + xy'z' + xyz$   
 $= z'y'(x'z' + xz) + xyz$   
 $= \underline{\underline{y'z'}} + xyz$

x	y	z	f
0	0	0	1
1	0	0	1

independent  
of  $x$  for this  
 $\therefore$  directly we  
can write  $\underline{\underline{y'z'}}$

$\therefore f = xyz' + xy'z' + xyz \rightarrow$  Canonical form  
 $f_1 = y'z' + xyz \rightarrow$  Not!  
 $f_2 = y'z' + xyz$

Check whether  $f_1$  &  $f_2$  are equivalent.

↳ Use canonical form

# Canonical form of switching function:-

→ All the terms contain all the variables ★ (either in normal or complementary)  
 $\underline{\underline{x}}$  or  $\underline{\underline{x'}}$

$f(x,y,z)$  →  $2^n$  terms (product form)  
 $\underbrace{x'y'z', xy'z', x'y'z', \dots}_{\star \text{ MINTERMS}}$

$$f_2 = y \cdot z' + x'yz$$

↳ sum of product

$$f = (\cancel{x}y + z), (\cancel{x}' + y' + z') \rightarrow \underline{\text{Product of sum}}$$

↓  
8 such terms  
MAX TERMS

→ MISSING → Shannon's expansion/decomposition theorem

# DeMorgan's Theorem for complementation:-

$$(x')' = x \rightarrow \text{Involution}$$

$$(x+y)' = x'y'$$

$$(x \cdot y)' = x'y'$$

Dual:-

$$\begin{array}{c} f(x_1, x_2, \dots, x_n, +, 1) \\ \downarrow \\ f_d(x_1, x_2, \dots, x_n, +, 0, 1) \end{array}$$

Dual & complement are different

# all switching expressions of a 2 variable functions:-

$$f(x, y) = a_0 xy' + a_1 x'y + a_2 xy + a_3 xy'$$

$$a_i \rightarrow 0/1$$

a <sub>0</sub>	a <sub>1</sub>	a <sub>2</sub>	a <sub>3</sub>
0	0	0	0
0	0	0	1
⋮	⋮	⋮	⋮
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

a <sub>0</sub>	a <sub>1</sub>	a <sub>2</sub>	a <sub>3</sub>	f(x, y)	Name
0	0	0	0	-	Inconsistency
0	0	0	1	f = x'y	AND
0	0	1	0	f = xy'	-
0	0	1	1	f = x	-
0	1	0	0	f = x'y	-
0	1	0	1	f = y	-
0	1	1	0	f = xy' + x'y	XOR
0	1	1	1	f = x + y	OR
1	0	0	0	f = x'y'	NOR
1	0	0	1	f = xy + x'y'	EQUIVALENCE
1	0	1	0	f = y'	NOT
1	0	1	1	f = y' + x	y → x Implication
1	1	0	0	f = x'	NOT
1	1	0	1	f = x' + y	x → y
1	1	1	0	f = x' + y'	NAND

# FUNDAMENTALS OF SWITCHING ALGEBRA

+ functionally complete set of operations:

(Canonical) form of switching expression:

$$\begin{aligned} \text{For SOP: } (n+y'z) &= n \cdot 1 + y'z \cdot 1 \\ &= n(y+y')(z+z') + y'z(z+z') \end{aligned}$$

$$f(x, y, z) = \overbrace{xyz + xy'z + xyz' + xy'z' + xyz' + xy'z'}^{\text{Canonical form}}$$

Canonical form

$$\begin{aligned} \text{For POS: } (x+y)(y'+z) &= (x+y+z \cdot z') (xz' + y'z) \\ &= (x+y+z)(x+y+z') (x'+y'+z)(x'+y'+z') \end{aligned}$$

(product term)

# Minterms  $\rightarrow xyz, x'y'z, \dots$

$$\text{SOP} = \Sigma(0, 5, 6, 7)$$

$x$	$y$	$z$	$xyz$	$x'y'z'$	$x'y'z$	$xy'z'$	$xy'z$	$xyz'$	$xyz$
0	0	0	-0	xyz					
0	0	1	-1						
0	1	0	-2						
0	1	1	-3						
1	0	0	-4						
1	0	1	-5	xy'z'					
1	1	0	-6						
1	1	1	-7	xyz					

$\rightarrow$  AND( $\cdot$ ), OR( $+$ ), NOT( $'$ )  $\{ \cdot, +, '\}$

A set of equations is functionally complete if any switching operation (SOP/POS) can be represented or realized by these operations

$$\{ \cdot, +, '\} / \{ \cdot, '\} / \{ +, '\}$$


$$\xrightarrow{\text{NAND}} \xrightarrow{\text{NOR}} \xrightarrow{\text{De Morgan}} (A+B)' = (A' \cdot B')'$$

Q. Show that NOR is functionally complete :-


$$\text{NOR} \rightarrow (A+B)'$$

Now, if  $A = B$ ,
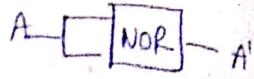
$$(A+A)' = A' \rightarrow \underline{\text{NOT}}$$




Now,

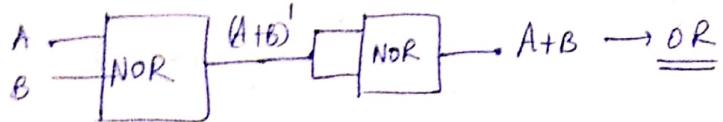

$\{+, 1\}$  can be generated  
∴ f.e.

Q. Show that  $f(A'B)$  is f.c. with 1.
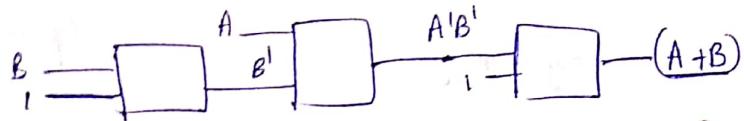
$$A \leftarrow \boxed{\quad} \rightarrow f(A', 1) = A' \rightarrow \underline{\text{NOT}}$$



Q. Check whether the given function is functionally complete or not.

Invert

$$\rightarrow f(x, y, z) =$$

$f(x, y, z) = \overline{x}y + \overline{y}z + \overline{z}x$

## # analogy between switching algebra & Boolean algebra

→ Defn: Boolean algebra is a distributive, complemented lattice  
It is commutative, associative and idempotent.  
over distributive &  
complement

→ Boolean algebra  $B$  is a set of variables  $\{a, b, c\}$   
& a set of operations  $\{+, \cdot\}$  that satisfies the  
properties of idempotent, commutative, ~~absorption~~ absorption,  
associative & mutually distributive.

There are two bounds ~~0~~ 0 (lowest) & 1 (highest)  
greatest.

It has a unary operation of complementation.

# complementation is unique:-

$$\begin{array}{l|l} a+b_1=1 & a+b_2=1 \\ a \cdot b_1=0 & a \cdot b_2=0 \end{array}$$

$$b_1 = b_1 \cdot 1 = b_1(a+b_2) = b_1 \cdot a + b_1 \cdot b_2 = b_1 \cdot b_2$$

$$b_2 = b_2 \cdot 1 = b_2(a+b_1) = b_2 \cdot a + b_2 \cdot b_1 = b_2 \cdot b_1$$

$\Rightarrow b_1 = b_2$  ∴ complementation is unique.

Q. Show that BA (Boolean algebra) satisfy DeMorgan's law

$$(a+b)(a'b') = 0$$

$$(a+b) + a'b' = 1$$

→ Will be true if  $a'b' = (a+b)'$

→ Will " "

$$(a+b) \cdot (a'b') = \underline{aa'b'} + \underline{ba'b'} = 0 + 0$$

$$(a+b) + a'b' = (a+b+a') \cdot (a+b+b') = \underline{\cancel{a+b}} \underline{(1+a)} (1) \\ = \underline{\underline{1}}$$

$$a+0 = a$$

$$a+a' = 1$$

$$a \cdot 1 = a$$

$$a \cdot 0 = 0$$

INCOMPLETE

(A, B, A, B)

$$\begin{cases} a+b=1 \\ a.b=0 \end{cases}$$

a	0	1	a+b
b	0	1	a+b
1	1	1	1
a	a	1	a+b
b	b	1	b

Boolean  
algebra

.	0	1	a	b'
0	0	0	0	0
1	0	1	a	b
a	0	a	a	0
b'	0	b	0	b

- \* Switching algebra is 2-valued Boolean algebra.
- 2 valued Boolean algebra is isomorphic to switching algebra

\* XOR  $\oplus$  CXOR =  $a \oplus y = ay' + a'y$

①  $\{A, B, C\}$

$A \oplus B = C$

$A \oplus C = B$

commutative :-  $A \oplus B = B \oplus A$

associative :-  $A \oplus (B \oplus C) = (A \oplus B) \oplus C$

distributive :-  $\{., \oplus\}$

$A \cdot (C \oplus B) = A \cdot C \oplus A \cdot B$

check distributive for  $\cdot, +, \oplus$

→ Chapter 3 exercise of Keshavri :-

3.3(d) Simplify

$$a + ab + a'b'c + ab'c'd + a'b'cd'e + \dots$$

$$\begin{aligned} a+a'b &\rightarrow a \cdot 1 + a'b \\ &\rightarrow a \cdot (1+b) + a'b \\ &\rightarrow a + ab + a'b \\ &\rightarrow a + (a+a') \cdot b \\ &\rightarrow a + b \end{aligned}$$

Now,  $a+a=a$

$$\therefore a'b + a'b = \underline{\underline{a'b}}$$

$$\begin{aligned} &\rightarrow a+a'b \\ &\rightarrow a+b \\ &\rightarrow (a'b)' \\ &+ (a'b)c \\ &\rightarrow a+ac \\ &\rightarrow a+a'ac \\ &\rightarrow a'ac+a'ac \\ &\rightarrow (a'b'c')' \\ &\rightarrow a+b+c \end{aligned}$$

$$\begin{aligned} &\rightarrow a+b+a'(b+b'c) + a'b'c'd + \dots \\ &\rightarrow a+b+\underbrace{a'b+a'c}_{a+b+c} + \dots \\ &\rightarrow a+b+c + \dots \end{aligned}$$

$$\rightarrow a+b+c+d+e + \dots$$

(3.4) Find by inspection the complement of the following  
 (b) & simplify.

$$\begin{aligned}
 & [(x+y+z'), (y+x'z'), (z+x'y')] \\
 = & x' \cdot (y+z) + \underbrace{(y' \cdot (x+z) + z' \cdot (x+y))}_{x'y' + x'z' + y'z + xz' + yz'} \\
 = & \underline{x'y} + \underline{x'z} + \underline{yz}
 \end{aligned}$$

(3.5) Validate

$$xy + x'y' + x'yz = xy'z' + x'y' + yz$$

$$\begin{aligned}
 \text{LHS} &= \left( \begin{array}{l} xy'z' / x'(y'z') \\ y(x+z) + x'y' \\ xy + x'y' + yz \end{array} \right) \quad \text{LHS} = \text{RHS}
 \end{aligned}$$

$$\begin{aligned}
 \text{RHS} &= \left( \begin{array}{l} xy'z' + yz + x'y' \\ y(xz' + z) + x'y' \\ y(x+z) + x'y' \\ xy + x'y' + yz \end{array} \right)
 \end{aligned}$$

(3.6) If  $AB' + A'B = C$  then show that  $AC' + A'C = B$

Ans To prove  $AC' + A'C = B$

$$\begin{aligned}
 AC' + A'C &\rightarrow A \cdot \overbrace{(AB' + A'B)}^{\text{XNOR}} + A' \cdot \overbrace{(AB' + A'B)}^{\text{XNOR}}
 \end{aligned}$$

$\xrightarrow{\text{XNOR}}$        $\xrightarrow{\text{XNOR}}$

$A(AB + A'B') + A'(AB' + A'B)$   
 $AB + 0 + 0 + A'B$   
 $B(A + A')$   
 $\underline{B}$

$\overline{A \oplus B}$   
 $\neg AB + A'B'$

(3.7) Find A, B, C, D by using the following equations

$$A' + AB = 0$$

$$AB = AC$$

$$AB + AC' + CD = C'D$$

$$A' + B = 0 \Rightarrow A' = 0, B = 0$$

$$\Rightarrow \underline{A = 1, B = 0.}$$

$$AC = 0 \Rightarrow \underline{\underline{C = 0}}$$

(A, B, C, D)

(1, 0, 0, 1)

$$0 + 1 + 0 = 1$$

$$\Rightarrow \underline{\underline{D = 1}}$$

(3.8) A safe has 5 locks  $w, x, y, z$ , of which must be unlocked for the safe to open. The keys to the locks are distributed among 5 executives in the following way:

A has key to locks	$w, x$
B	$y, z$
C	$w, y$
D	$x, z$
E	$w, z$

- ① Determine number of executives required to open the safe
- ② Who is "essential executive" without whom the safe can't be opened?
- ③ Find all ~~possible~~ combinations of executives that can open the safe.

exec	$w$	$x$	$y$	$z$
A	✓		✓	
B	✓			✓
C		✓		✓
D	✗		✓	✓
E	✓		✓	✓

$\{w, y\} \cup \{x, z\} = \underline{\underline{C, A, D / C, A, E}}$   
Date

$\boxed{C A D / C A E} \rightarrow \text{reqd.}$


③

Only C  
has w.

$\therefore \underline{\underline{C}} \text{ is essential executive}$

Valid combinations
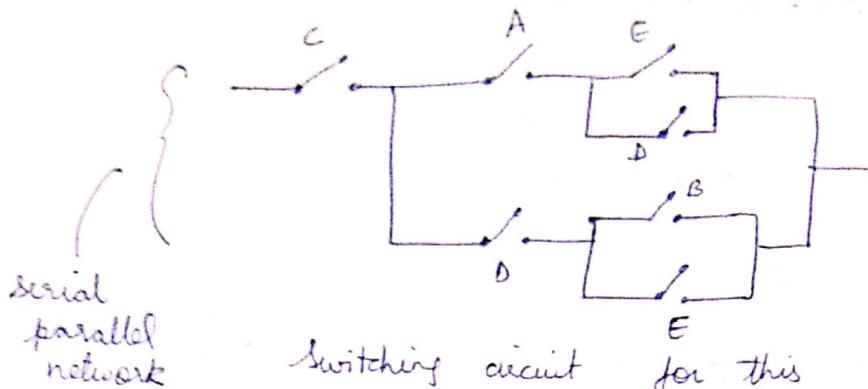
$$f(A, B, C, D, E) = CAE + CAD + CBD + CDE$$



### # Minimization of switching expression

Used algebraic properties to minimize the switching expression.

$$\begin{aligned}
 f(x_1, y, z) &= xyz' + x'yz' + yz \\
 &= yz' + yz \\
 &= y \quad \rightarrow \text{Irredundant \& minimal}
 \end{aligned}$$

→ Minimal expression → Cannot get another expression with fewer literals.

→ Irredundant expression. → Cannot be further reduced

1.) Minimum no. of literals

2.) Minimum no. of terms.

$$f = \sum (2, 0, 4, 3, 7, 5)$$

Truth Table

Input	Output
0 0 2	0 → 1
0 0 0	1 → 0
0 0 1	2 → 1
0 1 0	3 → 1
0 1 1	4 → 1
1 0 0	5 → 1
1 0 1	6 → 0
1 1 0	7 → 1
1 1 1	

$$f(x,y,z) = my_1' + my_2' + my_3' + z'y + xyz + zy'z$$

~~z'y + xyz + zy'z~~

~~xyz + zy'z~~

$$\textcircled{1} = my_1' + yz + my_1' \rightarrow \text{Redundant}$$

$$\textcircled{2} = z'y + yz' + xy \rightarrow \text{Redundant}$$

### Karnaugh Maps - Method of Minimization

$$\begin{aligned} & Aa + Aa' = A \\ \text{for } b,c,d & \quad A(a+a') = A1 + A \\ \text{say} & \quad \downarrow \\ & Aa + Aa' = A \end{aligned}$$

~~jd, jk, lk~~  
say

One bit varying

	00	01	11	10
0	1	0	1	1
1	1	1	1	0

	0	1
00	1	0
01	1	1
11	0	1
10	1	1

0	1	3	2
4	5	7	6

Adjacent  $\rightarrow$  Terms are varying in 1 literal.

Cube  $\rightarrow$  searching for 2 adjacent cells.

$\hookrightarrow 2^m$  cells  $\rightarrow$  ~~if  $m=1, 2, 3, \dots$~~

If it is a  $n$ -variable fn & we can identify a  $2^m$  cube then the minimized term have  $(n-m)$  literals.

$$x_2' + yz + yz' + zy'$$

$$yz' + xz + ny$$

# say, we have  $\rightarrow$

	00	01	11	10
0	0	1	1	1
1	1	0	1	1

$$y + xz + xz'$$

~~say~~ say  $f = \Sigma 4, 5, 6, 8, 12, 13, 14, 15$

ab	00	01	11	10	
cd	00	0	1	3	2
ab	01	4	5	7	6
cd	11	12	13	15	14
ab	10	8	9	11	10

ab	00	01	11	10	
cd	00	0	0	0	0
ab	01	1	1	0	1
cd	11	1	1	1	1
ab	10	1	0	0	0


$$f \rightarrow ac'd' + bc' + bd' + ab$$

AND-OR expression


ab	000	001	011	010	110	111	101	100
cd	000	0	0	0	0	0	0	0
de	00	0	0	0	0	0	0	0

$$\Rightarrow \text{NAND} \quad (A \cdot B)' = A' + B' \quad \text{OR, NOT}$$

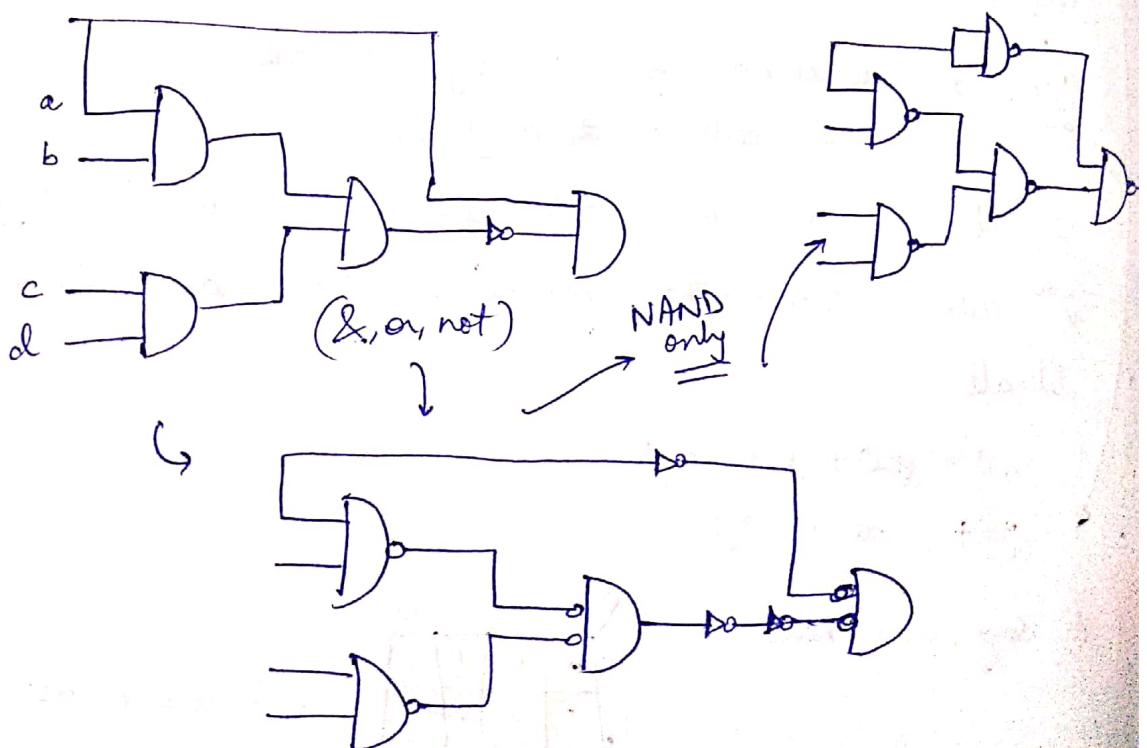
$$\Rightarrow \text{NOR} \quad (A+B)' = A' \cdot B' \quad \&, \text{NOT}$$



# Multiplexer :- Data selector

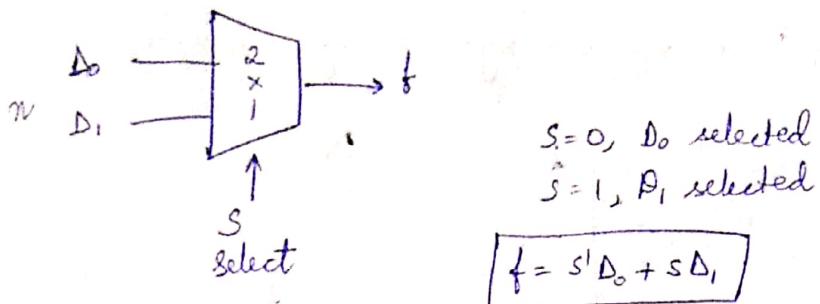

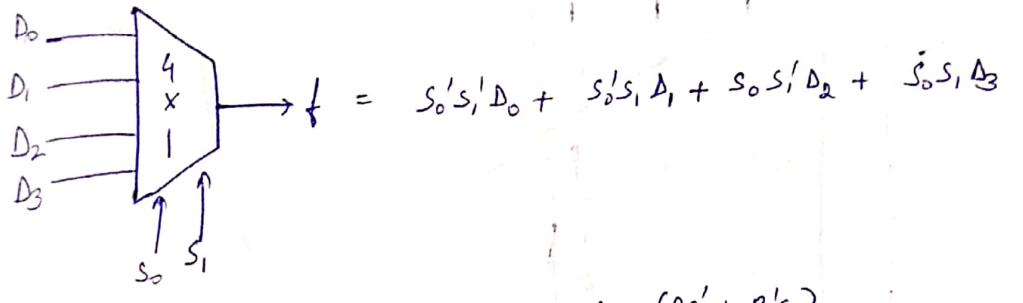If  $n$ -input variables,  $s = \log_2 n$





# Adder

$$f(A, B, C) = A \oplus B \oplus C = ABC + AB'C' + A'B'C + A'BC'$$


Consider 4x1 MUX
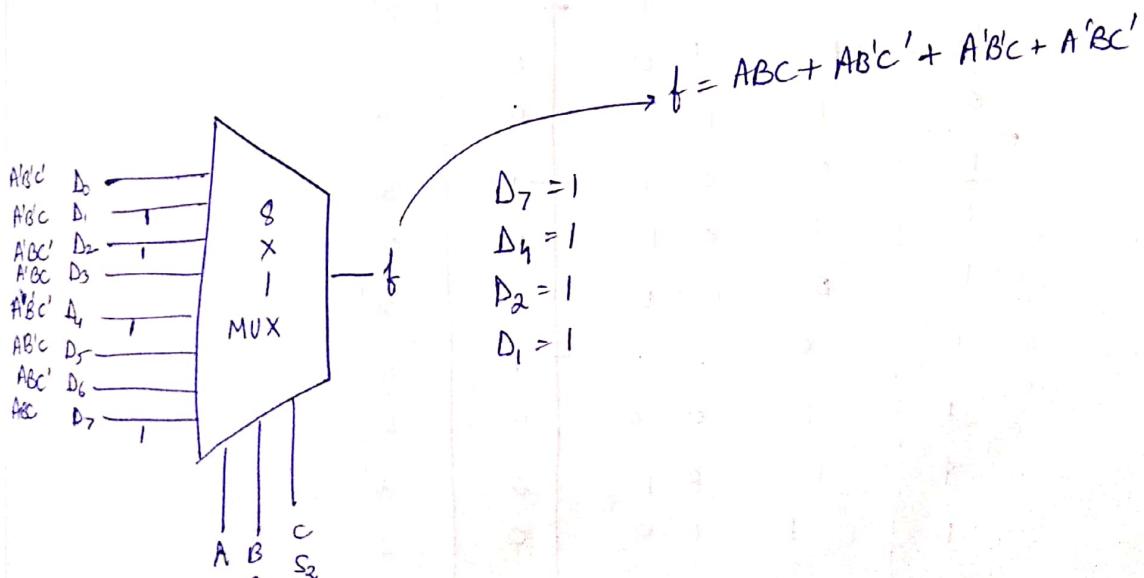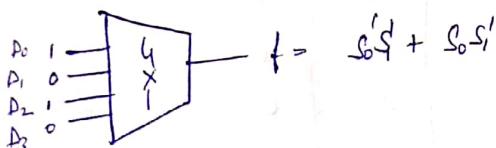
$$f = S_0'S_1'D_0 + S_0'S_1'D_1 + S_0S_1'D_2 + S_0S_1'D_3$$




→ For  $n$ -variable fn to be realized, we need  $2^n \times 1$  MUX  
(n-select 1)
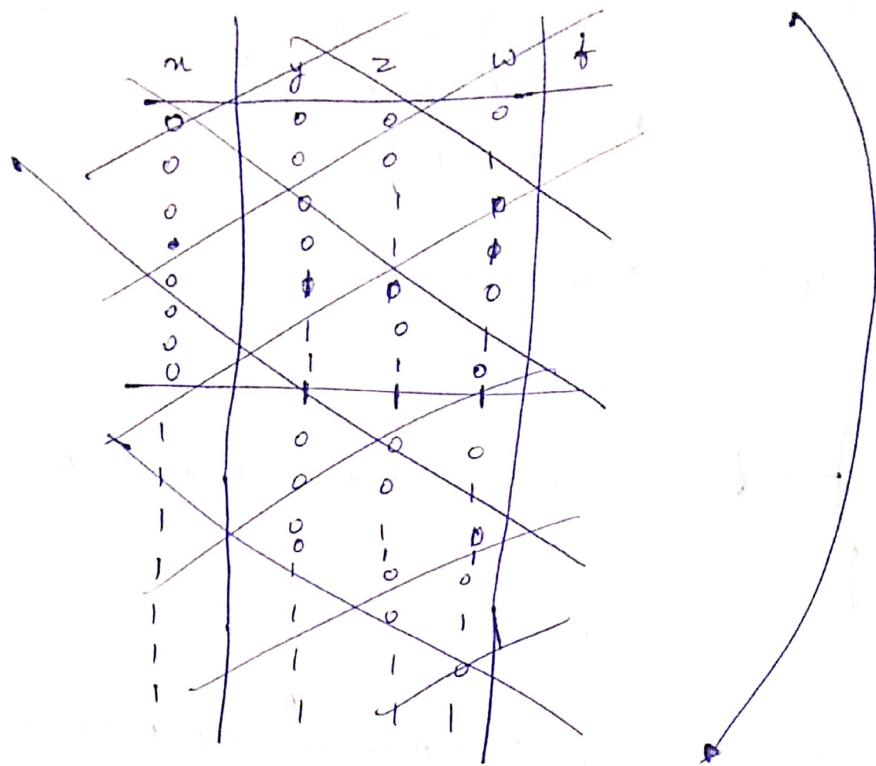
$$f(x, y, z, w) = xy'z'w' + xy'zw + xyz'w' + xyz'w + xyzw$$



x\y\z\w	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
f	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
f'	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0
x'	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	0
x	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1
w'	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
w	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1

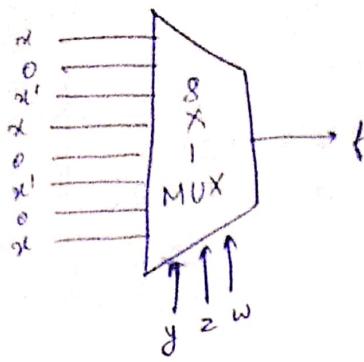

# Minimization with product of sum expression :-

	$wx'$	$wx$	$wz$	$wz'$
$xz'$	00	01	11	10
$xz$	00	01	11	10
$wz'$	00	01	11	10
$wz$	00	01	11	10

$$f = w'nyz' + w'nyz + \cancel{wxyz} \\ \cancel{wx'yz} + \cancel{wxyz'}$$

→ 4 product terms in 16 literals

SOP cheaper than POS, here.

$$(w'x')' = (w')' + (x')' \\ = w + x$$

Using POS →  $f = (w+x).(x+y).(w'+y+z) \cdot (w'+x'+z') \cdot (w+y+z)$ .  
 $(x'+y+z')$

# Something about DONT care condition → For invalid inputs, put any value, which reduces terms

& Implement  $\frac{\text{BCD}}{\text{Excess 3}}$  to excess 3 converter → Only for 0-9

Decimal	BCD	Excess 3
0	0000	0000
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100



P.T.O

so 10, 11, 12, 13, 14, 15

inputs can still be there. (here, they are invalid)

# K-Maps for $f_1, f_2, f_3, f_4$

$f_1 :=$

wz	yz	00	01	11	10
00	1	0	0	1	
01	1	0	0	1	
11		0	0	0	
10		1	0	0	

$$f_1 = w'z' + \bar{w}y'z'$$

Without dont care

With dont care:

wz	yz	00	01	11	10
00	1	0	0	1	
01	1	0	0	1	
11	X	X	X	X	
10	1	0	X	X	

Put  $x=1$  for  $\dots$ ,  
1 term only.

$$f_1 = \bar{z}'$$

Do for  $f_2, f_3, f_4$  with dont care.

$f_2 :=$

wz	yz	00	01	11	10
00	1	0	1	0	
01	1	0	1	0	
11	X	X	X	X	
10	1	0	X	X	

Put  $x=1$  for  $\dots$ ,

$$f_2 = y'z' + yz$$

$f_3 :=$

wz	yz	00	01	11	10
00	0	1	1	1	
01	1	0	0	0	
11	X	X	X	X	
10	0	1	X	X	

$$f_3 = x'y + \bar{x}z + \bar{y}z'$$

$f_4 :=$

wz	yz	00	01	11	10
00	0	0	0	0	
01	0	1	1	1	
11	X	X	X	X	
10	1	1	X	X	


$$f_4 = xz + xy + \cancel{w}$$

$$\therefore f_1 = \text{don't care}$$

$$f_2 = y'z' + yz$$

$$f_3 = xy'z' + yx'z + ux'z$$

$$f_4 = xz + xy + uw$$

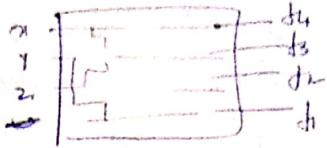

~~z → z'~~

Map-entered variable method for k-map:-

means  
for depends  
on A'

w'z'	00	01	11	10
wz'	1	(A)	A' 0	
wz	0	1	C 0	
y'z'	01	(A')	1 1 0	
yz'	11			
y'z	10	B	1 B' 1	
yz				

$$f(w, x, y, z)$$

$$f(w, x, y, z, A, B, C)$$

→ A & A' case treated as different variables

$$\therefore f = w'y^2 + w'w'y'z' + w'w'yz + w'w'y^2 + wwy^2$$

Now,

for A → make it 1.

other k-map variables → don't care (1's only)

other map-entered variables → 0 (A', B, B', C)

w'z'	x	(1 1) 0	
wz'	0	x 0 0	0
wz	0	x x 0	0
y'z'	0	x 0 x	

$$\rightarrow f_A = A \cdot w'w'z'$$

clearly,  $f_C = C \cdot u \cdot z$  (centre square)

$$f_{B'} = B' \cdot w \cdot z$$

$$f_B =$$

$\Rightarrow$  Map-entered variable. (use  $k = \text{map}$ )

- Step ① Put 0 in all the cells containing map-entered variable. Find the minimal expression using  $k = \text{map}$ .
- Step ② Now the fn f depends on A) Make all other map-entered variables 0. & make all 1's as don't care (Don't touch the zeroes) Then get a minimal expression using product of  $A \cdot f_A$
- Step ③ Repeat ② for other map-entered variables.

$$f = f_{k=\text{map}}(w, x, y, z) + \underline{\quad} A \cdot f_A + \underline{\quad} A' \cdot f_A' + \underline{\quad} B \cdot f_B + \underline{\quad} B' \cdot f_B' + \underline{\quad}$$

### # Quine-McClusky Method:

Switching or Boolean expression

Minimal expression

Irredundant expression  $\rightarrow$  can't be reduced further.

### Prime implicants:

Let  $f(x_1, x_2, \dots, x_n)$  &  $g(x_1, x_2, \dots, x_n)$  are two switching expressions functions.

Now,  $f$  covers  $g$ , if  $f$  contains a 1 everywhere where  $g$  does.  $\rightarrow f \geq g$

Now, if  $f$  covers  $g$  &  $g$  covers  $f$ , then  $f$  and  $g$  are equivalent.




Let  $h(x_1, x_2, \dots, x_n)$  be product term.

If  $f$  covers  $h$ , then it is said  $[h \rightarrow f]$ ,  $h$  is one implicant of  $f$ .

④ A prime implicant ( $P$ ) is a product term that implies the function  $f$  & dropping any literal from  $P$  produces another product term that does not imply  $f$ .
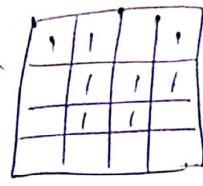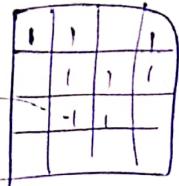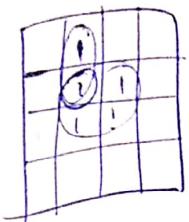
### # Essential prime implicant:

One prime implicant is essential if it covers a cell (min term) which is not covered by any other prime implicant.



→ Sum (Union) of all essential prime implicants is one of the irredundant expressions.

### # Theorem:

An irredundant Boolean expression is the sum(union) of all essential prime implicants.

Proof: Let  $f'$  be an irredundant expression which has one pre-implicant. If dropping  $P$  implies  $f'$  is still irredundant  $\Rightarrow$  literals can be reduced  $\Rightarrow$  expression can be reduced.  
Essential PI  $\Rightarrow$  Irredundant  
Prime Implicant  $\Rightarrow$  Minimal exp.

Quine-McCluskey

$$f = \sum_m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$$

Step 1	No. of 1's	group	wxyz
(0)	1	0	0 0 0 0
(1)	2	1	0 0 0 1
(2)	2	8	1 0 0 0

PTO

$$\Sigma \Rightarrow \{0, 1, 2, 5, 7, 8, 9, 10, 13, 15\}$$

Step 1

Index	Min term	w	x	y	z	Index ↴
0	0	0	0	0	0	No. of 1's in the term
1	1	0	0	0	1	
2	2	0	0	1	0	
3	8	1	0	0	0	
4	5	0	1	0	1	
5	9	1	0	0	1	
6	10	1	0	1	0	
7	7	0	1	1	1	
8	13	1	1	0	1	
9	15	1	1	1	1	

Step 2

Group of Min term

	w	x	y	z
0, 1	0	0	0	- ✓
0, 2	0	0	- 0	✓
0, 8	+	0	0	0 ✓
1, 5	0	-	0	1 ✓
1, 9	-	0	0	1 ✓
2, 10	-	0	1	0 ✓
3, 9	1	0	0	- ✓
8, 10	1	0	-	0 ✓
5, 7	0	1	-	1 ✓
5, 13	-	1	0	1 ✓
9, 13	-	1	0	1 ✓
7, 15	-	1	1	1 ✓
13, 15	1	1	-	1 ✓

Step 3

0, 1, 8, 9

w x y z

- 0 0 - A =  $x'y'$

0, 2, 8, 10

- 0 - 0 B =  $x'z'$

repeat 0, 8, 10, 2

11, 16, 17

1, 5, 9, 13

- - 0 1 C =  $y'^2$

5, 7, 13, 15

- 1 - 1 D =  $x^2$

No more minimizations possible.  $f = A + B + C + D$

# decimal representation Quin-McClusky:

1) Difference of ~~two~~ minterms with different indices is

power of 2. (1 bit difference)

2) If the minterm with smaller index is larger than the minterm with larger index, then it cannot be combined even if the difference between minterms is power of 2.

3) Minterms with same indices are not covered.

$$\therefore f(v, w, x, y, z) = \sum (13, 15, 17, 18, 19, 20, 21, 23, 25, 27, 29, 31)$$

$$+ \sum (1, 2, 12, 24)$$

→ Initially, we consider don't care as 1.

Step	Index	Minterms	Exp 2		Gives posn of $\rightarrow$ *
			1	2	
1	1				
2	2	12	1, 17	(16)	-A
	17		2, 18	(16)	-B
	18		17, 19 (2)	12, 13	(1)
	20		17, 21	(4)	-C
	24		17, 25	(8)	(17, 13) → X
3	3	13	18, 19	(1)	15, 31 (16)
	19		18, 21	(1)	23, 31 (8)
	21		18, 25	(8)	27, 31 (4)
	25		20, 21	(1)	29, 31 (2)
4	4	15	24, 25	(1)	
	23		13, 15	(2)	
	27		13, 29	(16)	
	29		19, 23	(4)	
	31		19, 27	(8)	
	39		21, 29	(8)	
	41		25, 29	(4)	

Step 3

Now, we check if differences match or not

$$\underline{17, 19, 21, 23} \quad (2, 4) \checkmark$$

$$17, 21, 25, 27 \quad (2, 8) \checkmark$$

$$\underline{17, 21, 25, 29} \quad (4, 8) \checkmark$$

$$13, 15, 29, 31 \quad (2, 16) G$$

$$19, 23, 27, 31 \quad (4, 8) \checkmark$$

$$21, 23, 29, 31 \quad (2, 8) \checkmark \text{ (Already covered)}$$

$$25, 27, 29, 31 \quad (2, 4) \checkmark$$

Step 4

$$17, 19, 21, 23, 25, 27, 29, 31$$

$$\underline{(2, 4, 8)} \rightarrow H$$

Max combination we can make

$A \rightarrow H$  are ~~not~~ prime implicants.

$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$
$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$

NOT essential prime implicants

Now, to find essential prime implicants:



$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 1 \\ 0 \\ 0 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 1 \end{smallmatrix}$
$\begin{smallmatrix} 1 \\ 0 \\ 1 \\ 1 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 1 \\ 0 \end{smallmatrix}$	$\begin{smallmatrix} 0 \\ 1 \\ 0 \\ 0 \end{smallmatrix}$

$v'wxyz'$	$\checkmark$							
$w'x'y'z'$	$A$	$X$	$.$	$.$	$.$	$.$	$.$	$.$
$w'xy'z'$	$B$	$X$	$.$	$.$	$.$	$.$	$.$	$.$
$v'w'x'y$	$C$	$X$	$.$	$.$	$.$	$.$	$.$	$.$
$v'w'x'y'$	$D$	$X$	$X$	$.$	$.$	$.$	$.$	$.$
$v'w'xy'$	$E$	$X$	$X$	$X$	$(\times)$	$X$	$X$	$X$
$vw'x'y'F$	$F$	$X$						
$wxz$	$G$	$X$	$(\times)$	$X$	$X$	$X$	$X$	$X$
$vz$	$H$	$X$	$X$	$X$	$X$	$(\times)$	$(\times)$	$(\times)$


$E, G, H \rightarrow$  essential prime implicant

B/D koi thi for 18

## 7-segment display

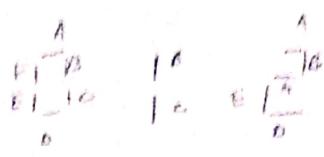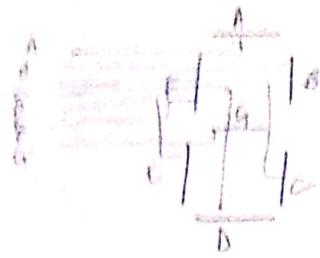

## B7D to 7-segment display

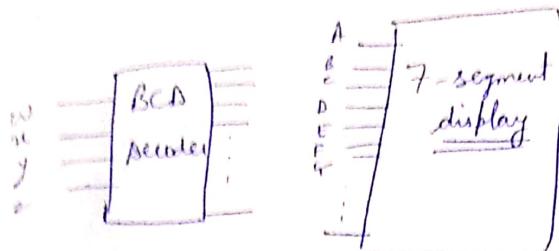

Decimal	BCD	A	B	C	D	E	F	G
	w x y z	f1	f2	f3	f4	f5	f6	f7
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	0	1	1	0	0	1	1
5	0 1 0 1	1	0	1	1	1	1	1
6	0 1 1 0	1	0	1	1	0	0	0
7	0 1 1 1	1	1	1	0	1	1	1
8	1 0 0 0	1	1	1	0	0	1	1
9	1 0 0 1	1	1	1	0	1	1	1

	y'z'w'	y'z'w	y'z'w'	y'z'w	y'z'w'	y'z'w	y'z'w'	y'z'w
00	1	0	1	1	0	1	0	1
01	0	1	1	1	0	1	0	1
11	1	1	0	0	1	1	1	1
10	1	1	0	0	1	1	1	1


$$f_1 = x'z' + y' + w + xz' \rightarrow \text{With don't care}$$

Don't care  
only if  
all inputs  
are 0-9  
otherwise 0. (0000)

Without don't care

	00	01	11	10
00	1 0	1 1	1	
01	0	1 1	1	
11	0	0	0	0
10	1 1	0	0	0

$$f_1 = w'y + xz + w'x'y' + x'y'z$$

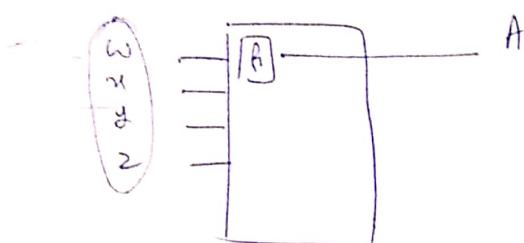

# Quin-McCluskey method of minimization:

$$f = \sum (1, 3, 4, 5, 6, 7, 10, 11, 12, 13, 14, 15, 18, 19, 20, 21, 22, 23, 25, 26, 27)$$

→ Minimal expression

→ Prime implicants

→ Essential prime implicants

We have already found  
prime implicants  
(assume)

2	1	3	4	5	6	7	10	11	12	13	14	15	18	19	20
w'x	A	-	x	x	x	x				x	x	x			
v'x	B	-	x	x	x	x			x	x	x	x			
v'y	C	-											x	x	
v'w'y	D	-											x	x	
w'x'y	E	-					x	x							
v'w'y	F	-					x	x			x	x			
r'y'z	G	x						x							
w'yz	H	x				x							x		
v'yz	I	-	x			x	x	x			x				
v'w'z	J	x	x	x	x	x	x	x				x			
vwx'z	K														x

One entry in column will  
mark, those p.i are e.p.i

A, B, J, K



	10	11	12	13	14	15	16	17	18 ✓	19 ✓	20 ✓	21 ✓	22 ✓	23 ✓	24 ✓	25 ✓	26 ✓
C	-	-	-	-	-	-	-	-	x	x	x	-	-	-	-	-	-
gC X D	-	-	-	-	-	-	-	-	x	x	-	-	-	-	-	-	-
E	-	x	x	-	-	-	-	-	-	-	-	-	-	-	-	-	x
gC F	-	x	x	-	-	-	-	-	-	-	-	-	-	-	-	-	-
G	-	-	x	-	-	-	-	-	-	-	x	-	-	-	-	-	-
H	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-
I	-	-	-	x	-	-	-	-	-	-	-	-	-	-	-	-	-
C, E	↑	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-

$$\Rightarrow f(v, w, x, y, z) = \underbrace{A + B + \sigma + K}_{\text{prime implicants}} + C + E.$$

$$\begin{array}{ccccc} v & w & x & y & z \\ 0 & 1 & - & - & - \\ 0 & 1 & - & - & - \\ 1 & 1 & 1 & 1 & 1 \end{array}$$

	21	22	23	24	25	26 ✓	27 ✓	A	B	C	D	E	F	G	H	I	J	K
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	
x	-	x	x	-	-	x	x	-	-	-	-	-	-	-	-	-	-	

$$\begin{array}{ccccc} v & w & x & y & z \\ 1 & 1 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 & 1 \\ \hline v & w & x' & z' & \end{array}$$

A - k  
prime  
implicants

	0	1	3	4	7	13	15	19	20	22	23	29
A					x	x						x
B	x				x	x						x
C		x		x				x				x
D										x	x	
E									x	x		
F			x						x			
G		x	x									
H	x			x								
I	x	x										

A (13, 15, 29, 31)

B (7, 15, 23, 31)

C (3, 7, 19, 23)

D (22, 23)

E (20, 22)

F (4, 20)

G (1, 3)

H (0, 4)

I (0, 1)

(3)

0 1 4 20 22

No essential  
P is here,  
so →

Now to reduce:

$$P = (H+I) \cdot (G+I) \cdot (F+H) \cdot (E+F) \cdot (F+G+H)$$

$\underbrace{H+I}_{\text{covers } 0}$      $\underbrace{G+I}_{\text{covers } 1}$      $\underbrace{F+H}_{\text{covers } 4}$      $\underbrace{E+F}_{\text{covers } 20}$      $\underbrace{F+G+H}_{\text{covers } 22}$

$$(I+G \cdot H) \quad (E+DF) \quad (F+H)$$

$$= (FI + HI + FI \cdot GH + GH) \cdot (E+DF)$$

$$= (FI + HI + GH) \cdot (E+DF)$$

$$= \cancel{FI} + \cancel{HI} + \cancel{GH} +$$

$$\cancel{DFI} + \cancel{DFHI} + \cancel{DGH}$$

$$\begin{aligned}
 f &= A + C + \cancel{EFI} & \checkmark \\
 &\quad \vdots & \checkmark \\
 &\quad \cancel{GHI} & \checkmark \\
 &\quad \cancel{EGH} & \checkmark \\
 &\quad \cancel{DFI} & \checkmark \\
 &\quad \cancel{DFGH} \rightarrow X & \xrightarrow{\text{more literals}}
 \end{aligned}$$

## # Combinational circuit design:

Present output depends on present input


## # Sequential circuit design :-

Present output depends on present input & past history.


## # Arithmetic Logic unit:-

$+,-,\times,/,<,>,\&, \mid$

→ Design of 1 bit ALU.      &, |, sum

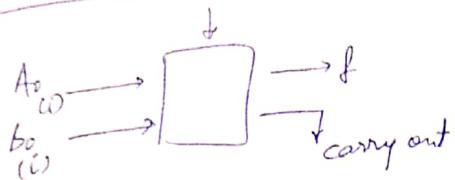


16 bit  
 $i \in \{0 \rightarrow 15\}$


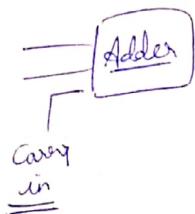



A	B	Carry out	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

## Half adder:

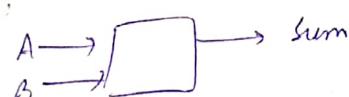

## Full adder:

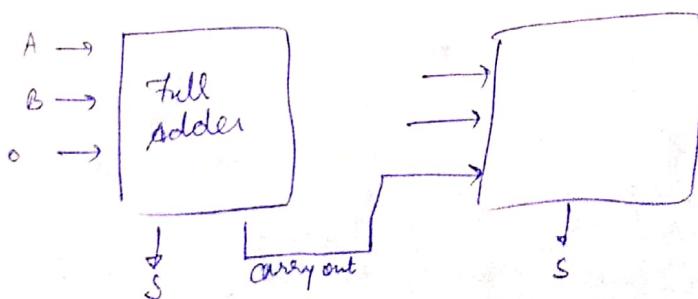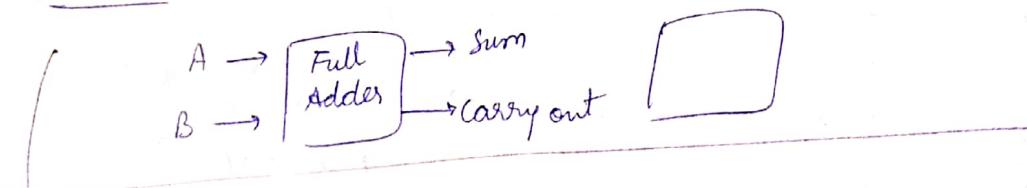

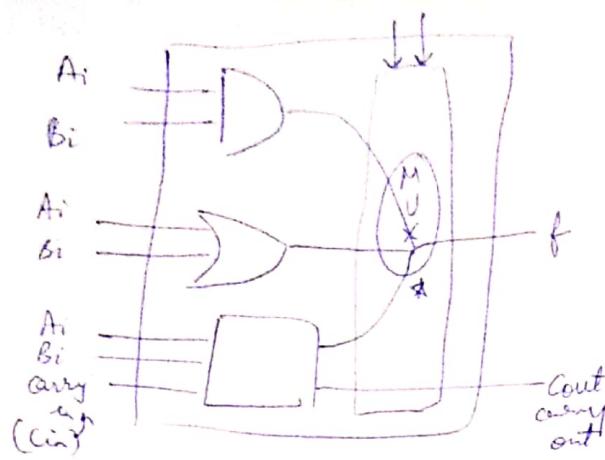

Map & get

Sum =  $A \oplus B \oplus C$

Make Karnaugh Map

A	B	C <sub>in</sub>	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

↓  
Make Karnaugh Map to get

$$\text{Cout} = AB + BC + CA$$

$$\therefore \text{Adder} \rightarrow \text{Sum} = A \oplus B \oplus C$$

$$\text{Cout} = AB + BC + CA$$

Control

00

&

01

or

10

Add/Sub (with add control / inv)

11

XOR



$$A + B$$

$$\rightarrow A + (-B)$$

( $\hookrightarrow A + (2^{\text{th}} \text{ comp of } 1's)$ )


( $\hookrightarrow A + (1^{\text{st}} \text{ comp of } B+1)$ )

$A + \text{inv}B + 1$

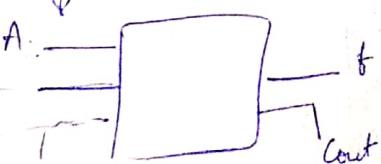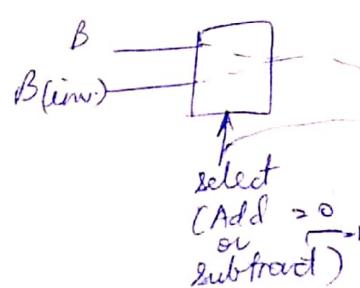


$f = 0 \text{ or } 1, \text{ depending on } + \text{ or } -$
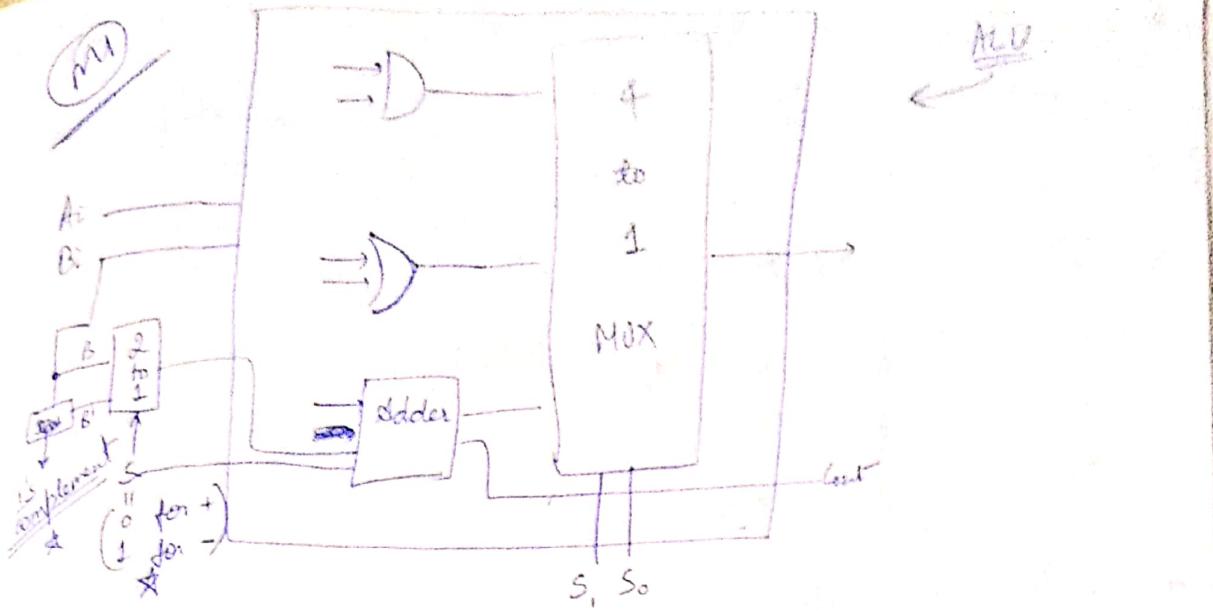
$$a_0 b_0 + a_1 b_1 A B + a_2 b_2 A B + a_3$$



$S_1, S_0$	
0 0	And
0 1	or
1 0	Add/Sub
1 1	XOR

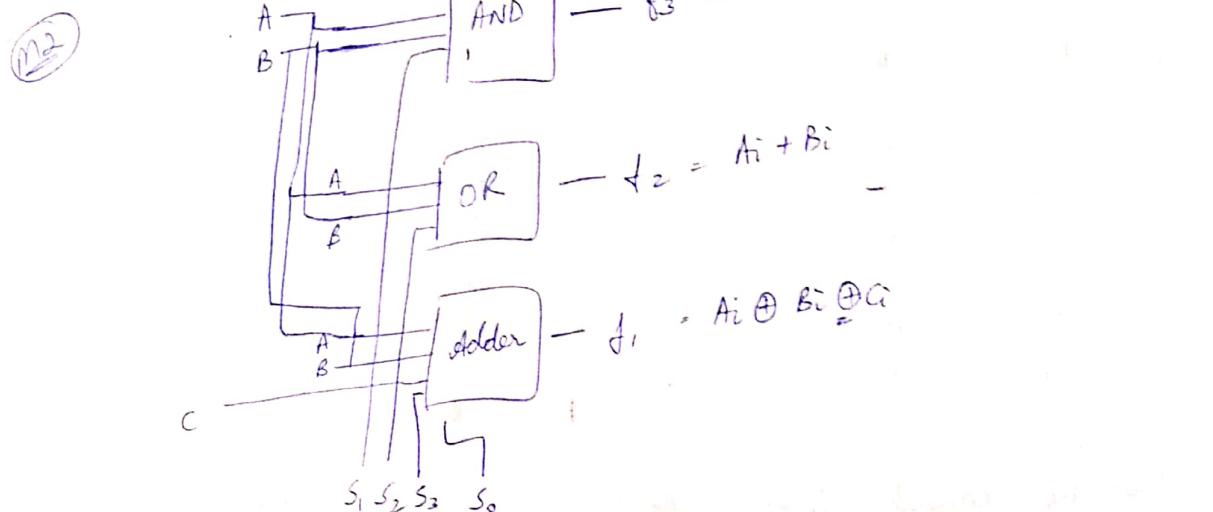

$$f = \underbrace{S_3 \cdot f_3}_{S_3 \cdot S_1} + \underbrace{S_2 \cdot f_2}_{S_2 \cdot S_0} + \underbrace{S_1 \cdot f_1}_{S_1 \cdot S_1} + S_0 \cdot f_0$$

Read about 2 var fns

$$\underline{\underline{S_0 S_1}}$$

# Combinational circuit design

( Comparator )

$\leq, =, \geq$

MSI - few  
LSI - few dozen  
VLSI - > 10000

→  $i^{\text{th}}$  stage 1 bit ALU:

$$\begin{array}{l|l|l} n=y & f_2 = x_1 y_1 + \overline{x_1} y_1' & (x_1 \oplus y_1) \\ (x > y) & f_1 = x_1 y_1' \\ (x < y) & f_3 = x_1' y_1 \end{array}$$

⇒ 2-bit comparator

$x$	$y$	$x > y$	$x = y$	$x < y$
$x_1 x_2$	$y_1 y_2$	$f_1$	$f_2$	$f_3$
00	00	0	1	0
00	01	0	0	1
00	10	0	0	1
00	11	0	0	1
01	00	1	0	0
01	01	0	1	0
01	10	0	0	1
01	11	0	0	1
10	00	1	0	0
10	01	1	0	0
10	10	0	1	0
10	11	0	0	1
11	00	1	0	0
11	01	1	0	0
11	10	1	0	0
11	11	0	1	0

⇒ We cannot take don't care, same reason as previous time

→ We can make Karnaugh map we can make for all  $f_1, f_2, f_3$  @ once only.

$y_1 y_2$	00	01	11	10
$x_1 x_2$	00	2	3	3
01	1	2	3	3
11	1	1	2	1
10	1	1	3	2

2 = 1 for  $f_2$

3 = 1 for  $f_3$

1 = 1 for  $f_1$

$$\rightarrow f_1 = x_1 y_1 + x_2 y_1' y_2 + x_1 x_2 y_2' = x_1 y_1 + x_1 y_2 (x_2 + y_2')$$

$$\rightarrow f_2 = x_1 x_2 y_1' y_2' + x_1' x_2 y_1' y_2 + x_1 x_2 y_1 y_2 + x_1' x_2' y_1 y_2'$$

$$= x_1 y_1' (x_2' y_2' + x_2 y_2) + x_1 y_1 (x_2 y_2 + x_2' y_2')$$

$$= (x_1 y_1' + x_1 y_1) \cdot (x_2' y_2' + x_2 y_2)$$


$$\rightarrow f_2 = (\overline{x_1 \oplus y_1}) \cdot (\overline{x_2 \oplus y_2})$$

$$\Rightarrow f_3 = x_1 y_1 + x_1 x_2' y_2 + x_2' y_1 y_2$$

$$= \underline{x_1 y_1} + \underline{x_2' y_2 (x_1' + y_1)}$$

$\Rightarrow$  So, we are not getting any definite repetition here,  
since we require knowledge of previous input (MSB side)  
(memory)

So, we construct like this:


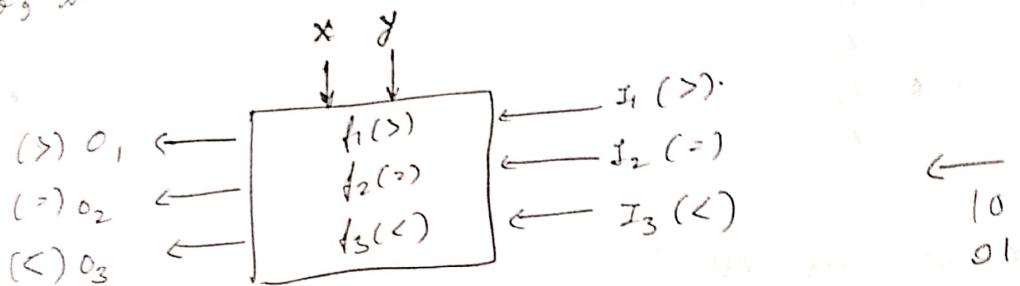


$$o_1 = f_1 \cdot I_1 + f_2 \cdot I_2 + f_3 \cdot I_3$$

$$o_2 = I_2 \cdot f_2$$



$$o_3 = f_3 + f_2 \cdot I_3$$

8 bit computer

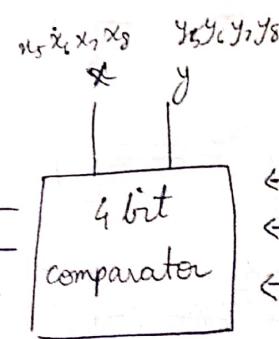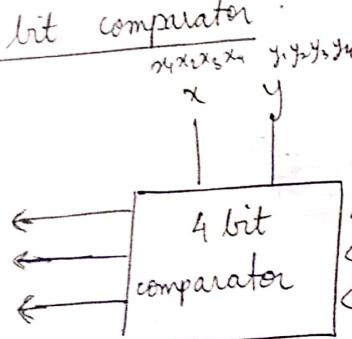

For 4 bit comparator, the simplification is better, so we use like this.

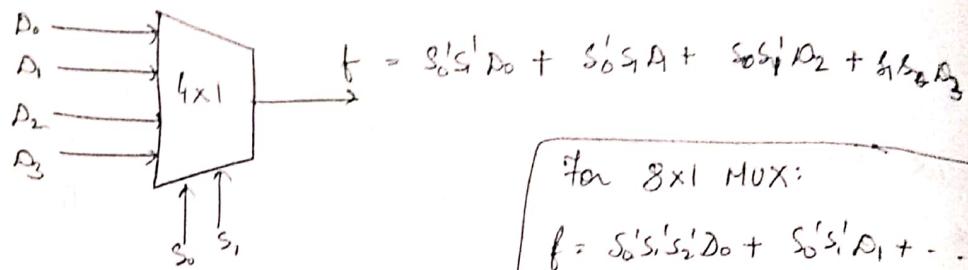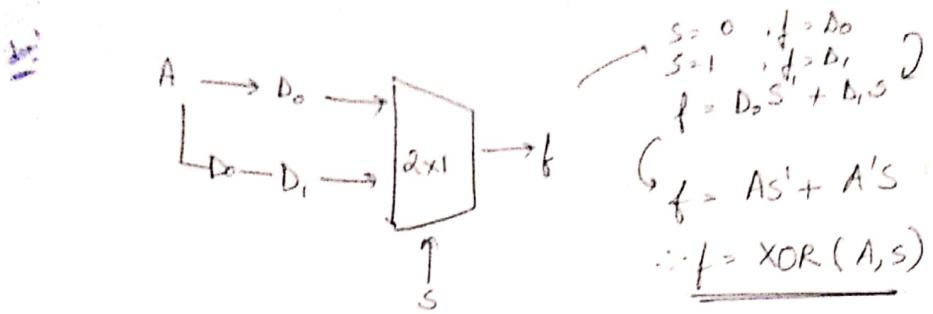Multiplexer can be used to realize all gates





$S_0$	$S_1$	$f$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$


for 8x1 MUX:  
 $f = S_0' S_1' S_2' D_0 + S_0' S_1' D_1 + \dots$

8 terms

# Circuit for MUX:

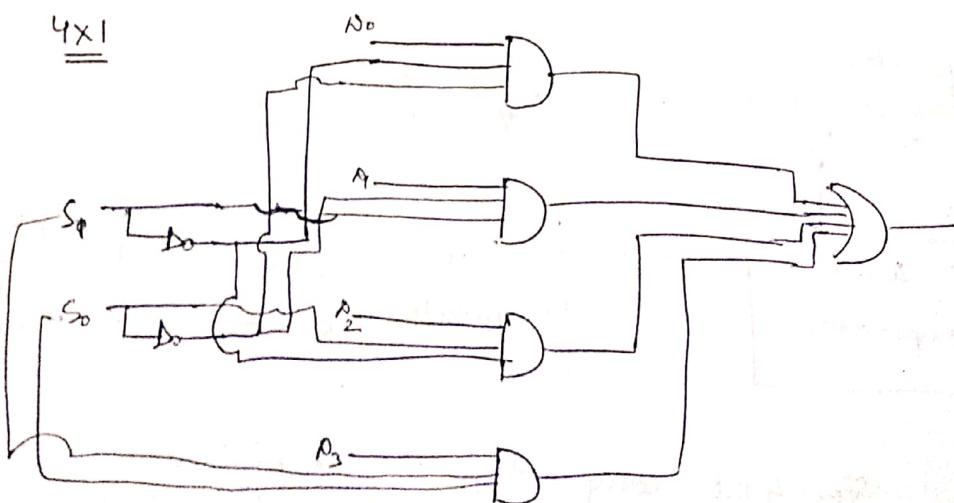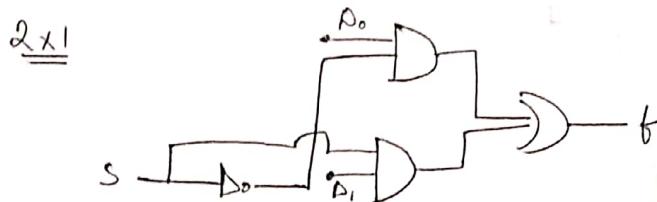

# 4x1 MUX using 2x1 MUX

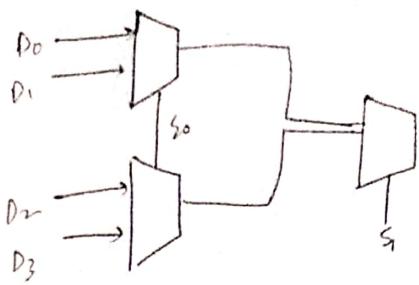

As req.


S, S0	P
00	P0
01	P1
10	P2
11	P3

Combinational circuit design:

- Multiplexer
- Priority encoder
- Decoder

→ 2 input NAND (NOR)?


Realize all gates using multiplexer.

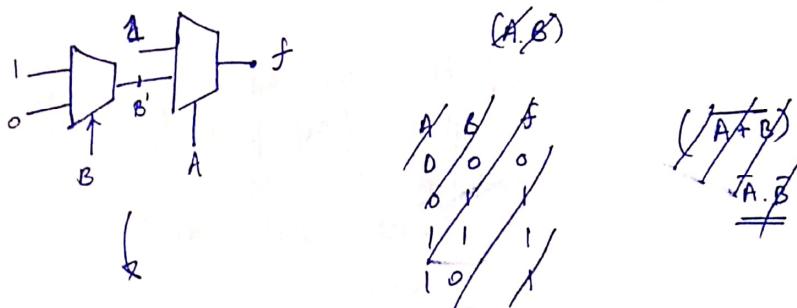

A	B	f
0	0	1
0	1	1
1	0	1
1	1	0

NAND


# Priority encoder:-

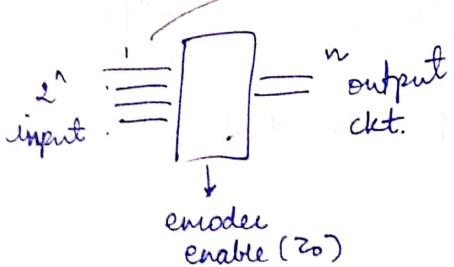

say, I want to give higher priority to some input lines.

Input lines -  $p_i$   
If  $i > j$ , then input  $p_i$  has higher priority than  $p_j$ .

Ex:  $n=3$

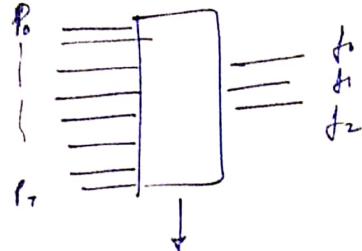

$P_0$	$P_1$	$P_2$	$P_3$	$P_4$	$P_5$	$P_6$	$P_7$	$f_0$	$f_1$	$f_2$	$\Sigma$
1	0	0	0	0	0	0	0	0	0	0	0
φ	1	0	0	0	0	0	0	0	0	1	0
φ	φ	1	0	0	0	0	0	0	1	0	0
φ	φ	φ	1	0	0	0	0	0	1	1	0
φ	φ	φ	φ	1	0	0	0	1	0	0	0
φ	φ	φ	φ	φ	1	0	0	1	0	1	1
φ	φ	φ	φ	φ	φ	1	0	1	1	1	0
φ	φ	φ	φ	φ	φ	φ	1	1	1	1	1

$\phi \rightarrow$  dont care

↳ Wade wale ko  
higher priority  
dena hai, so  
lower wale dont  
care.

$$f_0 = \underbrace{P_4 P_5' P_6' P_7'} + \underbrace{P_5 P_6' P_7'} + \underbrace{P_6 P_7'} + P_7$$

$$f_0 = P_4 + P_5 + P_6 + P_7$$

$$(P_6 + P_7)' = P_5'$$

$$f_1 = P_2 P_3' P_4' P_5' P_6' P_7' + P_3 P_4' P_5' P_6' P_7' + P_6' P_7 + P_7$$

$$= P_4' P_5' P_6' P_7' (P_2 + P_3) + P_6 + P_7$$


$$\hookrightarrow (\underline{P_4' P_5' (P_2 + P_3)} + P_6 + P_7) ?$$

$$f_2 = P_1 P_2' P_3' P_4' P_5' P_6' P_7 + P_3' P_4' P_5' P_6' P_7' + P_5 P_6' P_7' + P_7$$


- Minimize

Make combinational circuit using  
&, |, not. Ex:

# Decoder:

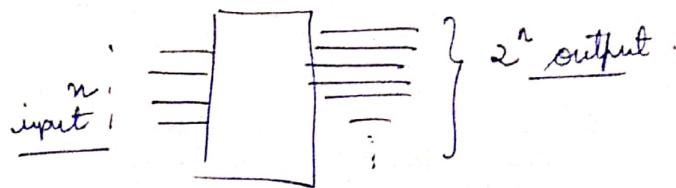

$$n \rightarrow 2^n$$

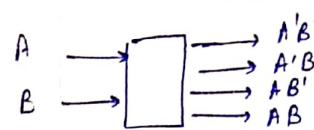


for memory  $\rightarrow$  Memory address decoder.




$\Rightarrow 2^n$  data

decoder  
only.


#  $\rightarrow$  2 to 4 decoder

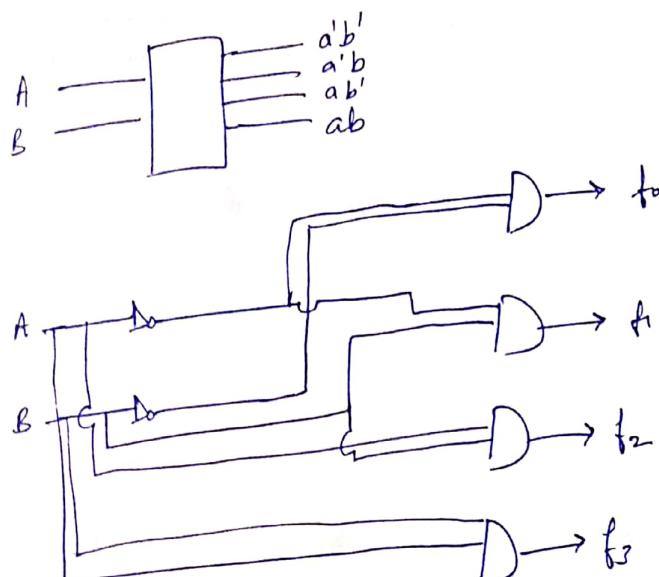


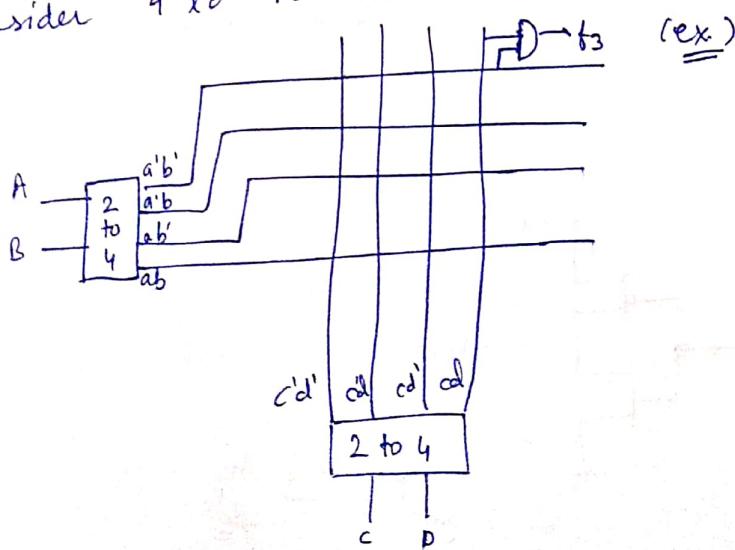
Now, we need VLSI type design (i.e., extendable design)  
∴ consider 4 to 16 decoder:-




# CMOS :

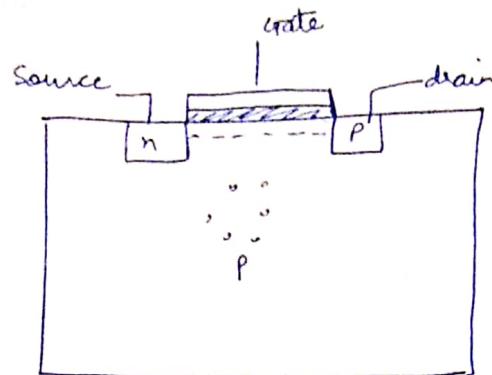

n-mos :

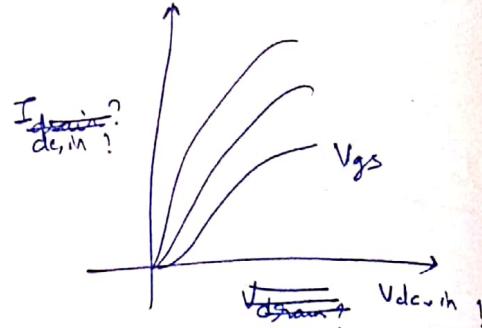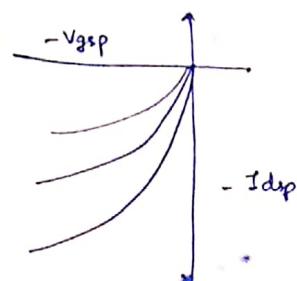


Switch :- nmos, pmos, cmos can be used.

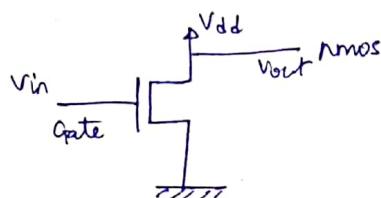


Power consumption is there if  $V_{dd}$  is ground connection we get:

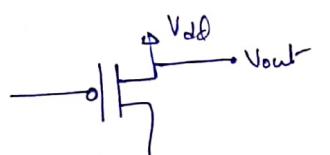If  $V_{in} = 0 \Rightarrow$  n-mos is off  $\Rightarrow V_{out} = \text{high}$   
 $V_{in} = 1 \Rightarrow$  n-mos on,  $\Rightarrow V_{out} = 0$  Ground




$\rightarrow V_{in} = 1, V_{out} = 1.$   
 $V_{in} = 0, V_{out} = 0.$

CMOS

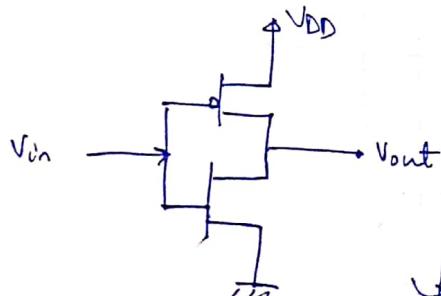


NOT  
by def.

### # 2-input NAND

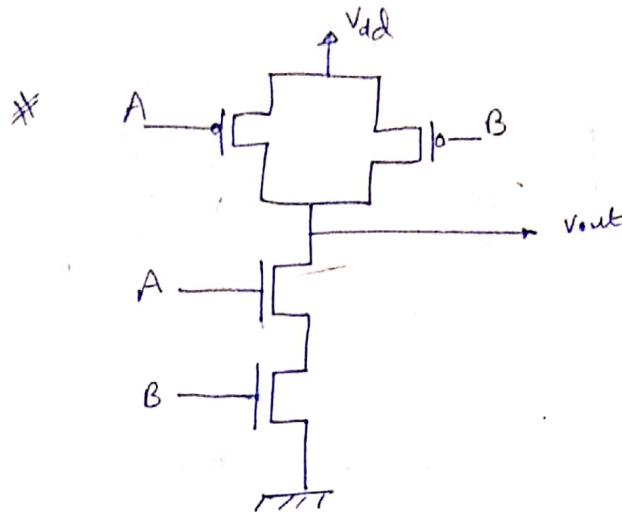


A	B	Vout
0	0	1
0	1	1
1	0	1
1	1	0

NAND

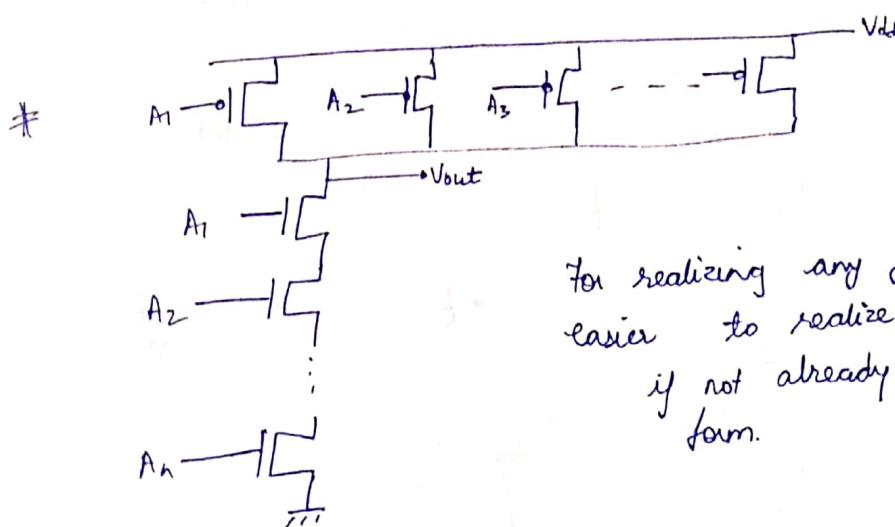


for realizing any fn, it is easier to realize its N-counterpart, if not already in that form.

### # NOR

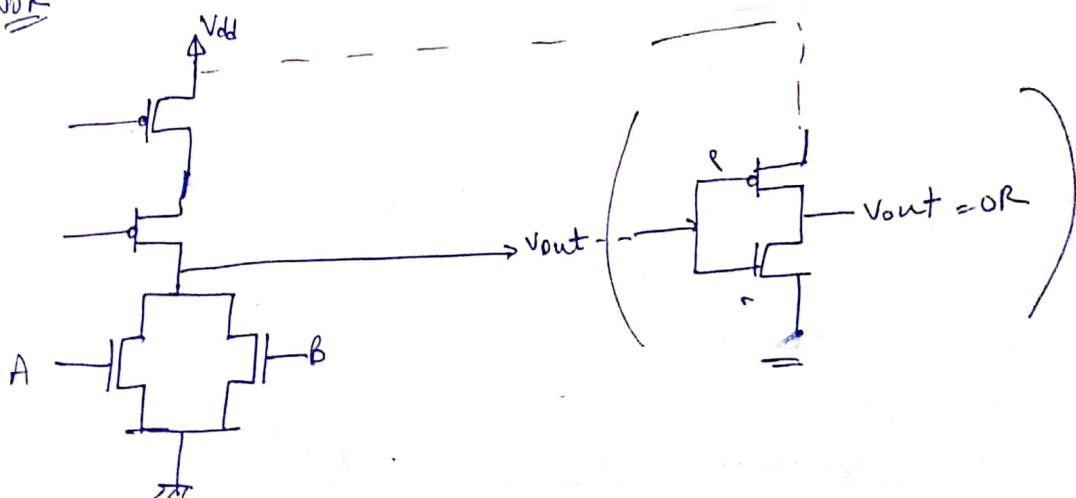

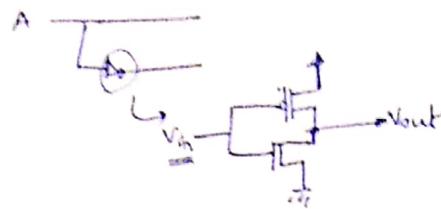
A ka  $\bar{A}$  den ke liye bhi CMOS use kar sakte hain



$$f = AB + \bar{A}C + D$$

$$\downarrow (\bar{f}) = \overline{(AB + \bar{A}C + D)} = \overline{(\bar{A} + B)(A + \bar{C})(\bar{D})}$$

Implement this

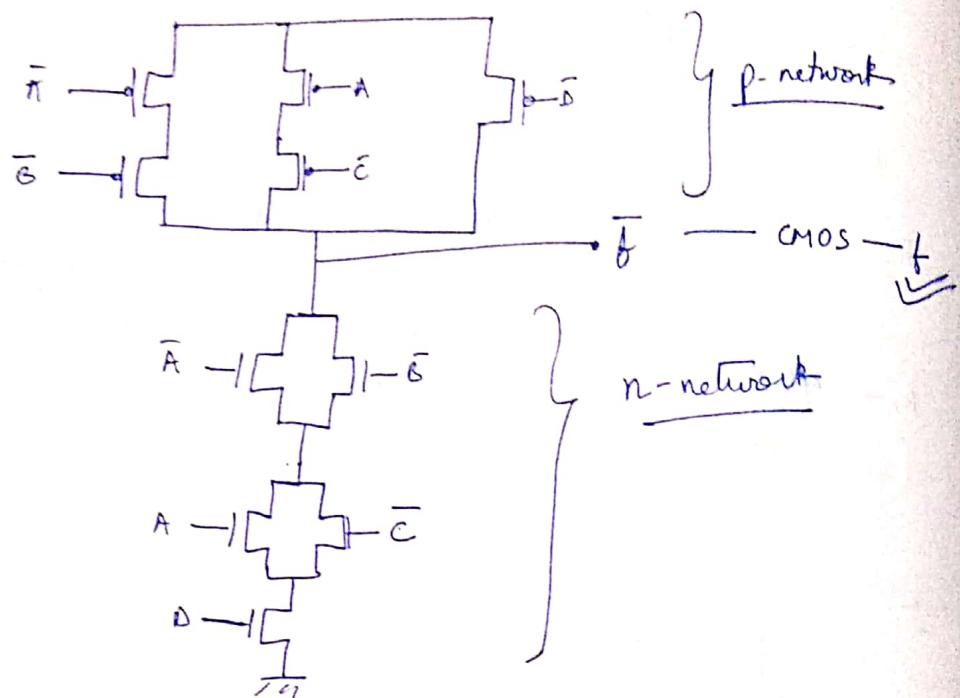


p-network is dual of n-network



& — OR

OR — &

Generally  $(f) \rightarrow$


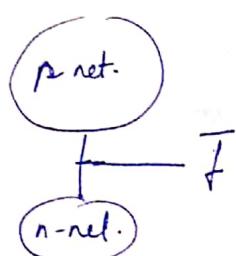

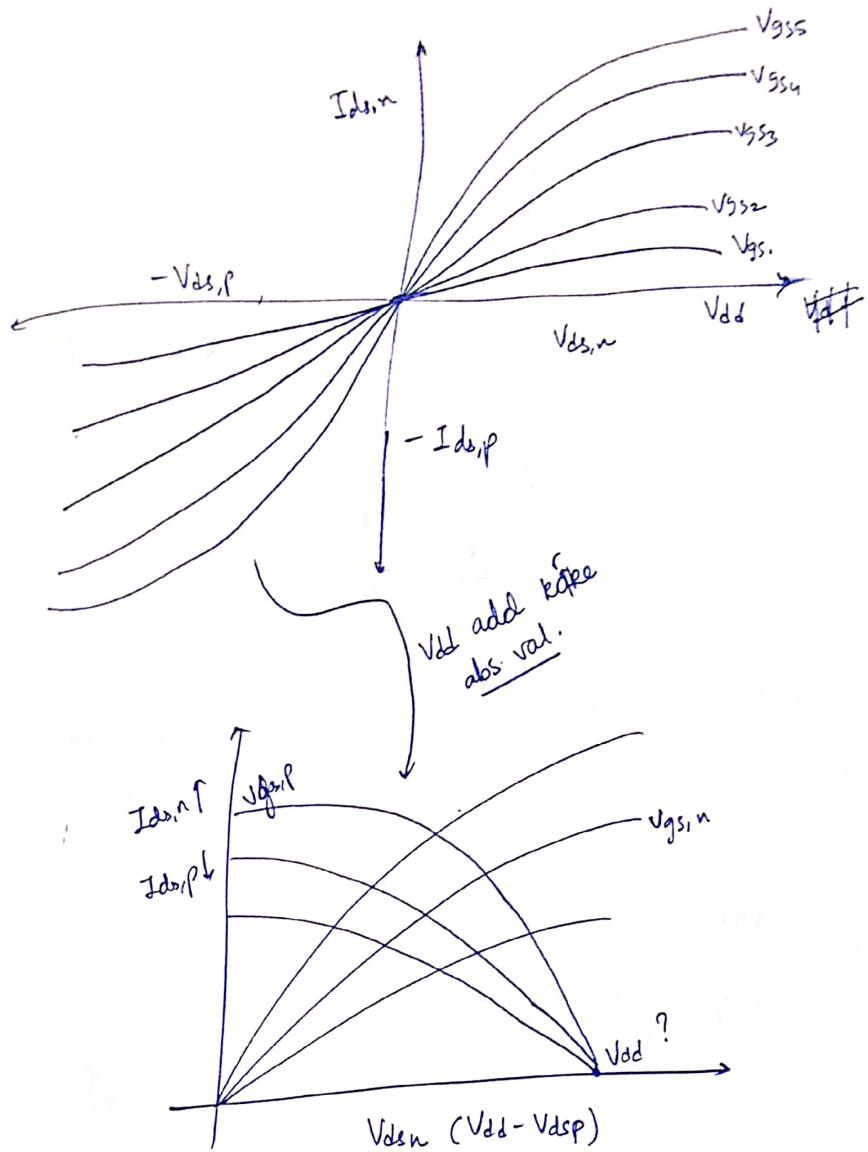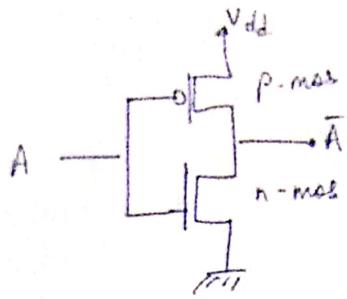
## # DC Characteristics of NOT (CMOS inverter) :-



$$V_{gs,n} (= V_{gs,p}) = V_{in}$$

$$I_{ds,n} = I_{ds,p}$$

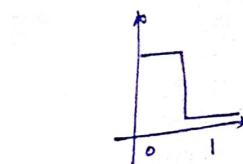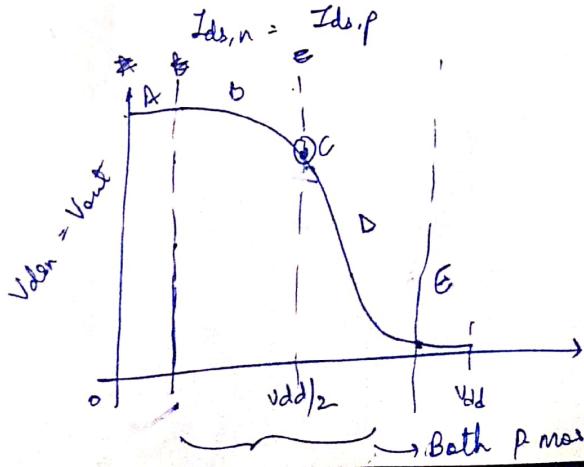

Coupled PTO

Region A: pmos is on (saturated)  
nmos is in cutoff (on)

check?


Region B,C,D: pmos on, nmos on, ~~region~~

Region E: n is in saturated  
p is in cutoff

C  
calibration

C-transition fit.
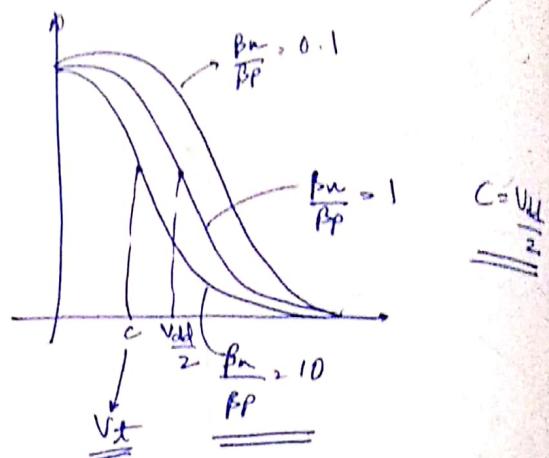
$$\Rightarrow \beta_{nL} = \left( \frac{ne}{t} \right) \left( \frac{w}{L} \right)$$



$$0 - V_t \rightarrow 0 \\ V_t - V_{dd} \rightarrow 1$$

$$\begin{pmatrix} 0 - 2.5 \rightarrow 1 \\ 2.5 - 5 \rightarrow 0 \end{pmatrix}$$

# Noise Margin: (NM)

$$NML_{low} = | V_{IL\min} - V_{OL\min} |$$

$$NM_{H\min} = | V_{OH\max} - V_{IH\max} |$$

# Adder

$$\begin{array}{r}
 A \quad 1 \ 0 \ 1 \ 1 \ 1 \ 0 \\
 B \quad 1 \ 0 \ 1 \ 1 \\
 \hline
 C_{out} \quad S \quad 1 \ 0 \ 0 \ 0 \ 1
 \end{array}$$

$S = A \oplus B \oplus C_{in}$   
 $C_{out} = AB + BC_{in} + C_{in}A$

$S = A'B'C_{in} + A'B'C_{in} + A'BC_{in} + ABC$   
 Reduce / Minimize  
 to get  $A \oplus B \oplus C_{in}$

$C_{out} = A'B'C_{in} + A'B'C_{in} + AB'C_{in} + ABC$   
 $= \underbrace{AB + BC}_{=} + CA \quad \Rightarrow \quad \underbrace{(A+B) \cdot C}_{=} + AB \quad \Rightarrow \quad \& \text{ reduced}$

We need  $\Delta$ , OR,  $A, A'$   
 (complemental input).

Reducing the hardware  $\Rightarrow$  Reduce area

Time  
 Power  
 Main prob.


challenges

$\Rightarrow$  for  $S = (A'B'C_{in} + \dots)$   $\Rightarrow$  4-3 inp 4 gates  
 $\qquad\qquad\qquad$  1-4 inp OR gates


$$\begin{aligned}
 &= (A+B+C)(AB + C(A+B))' + ABC \\
 &= (A+B+C) \cdot (A'+B') \cdot (A'+C') \cdot (B'+C') + ABC \\
 &= (AB' + A'B + B'C) \cdot (A'B' + A'C' + B'C' + C') + ABC \\
 &\qquad\qquad\qquad + A'C \\
 &= AB'C' + A'BC' + A'B'C + ABC
 \end{aligned}$$

Trying to represent such terms from  $C_{out}$  to reduce hardware

Now,  $C_{out} \Rightarrow$

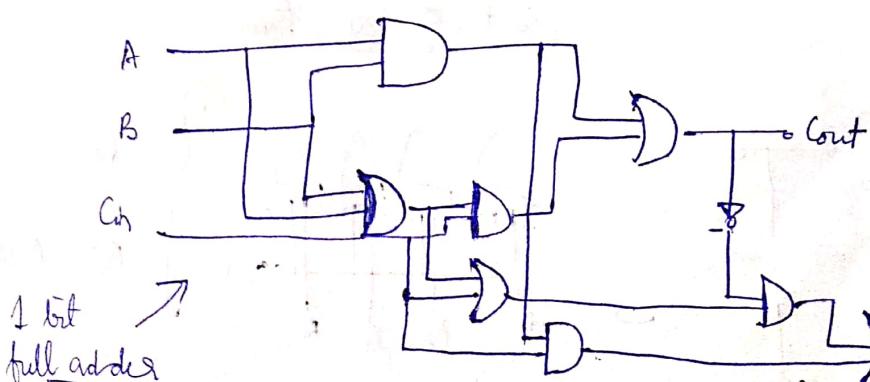


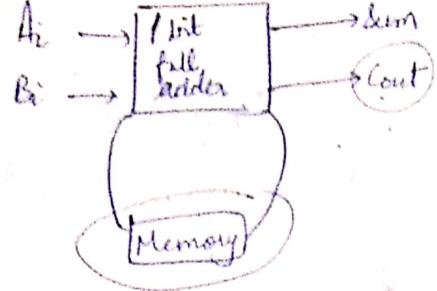$\Rightarrow$  4 2-inp  
 $\Rightarrow$  4 2-inp OR  
 $\Rightarrow$  1 NOT  
 Sum



Serial adder :-
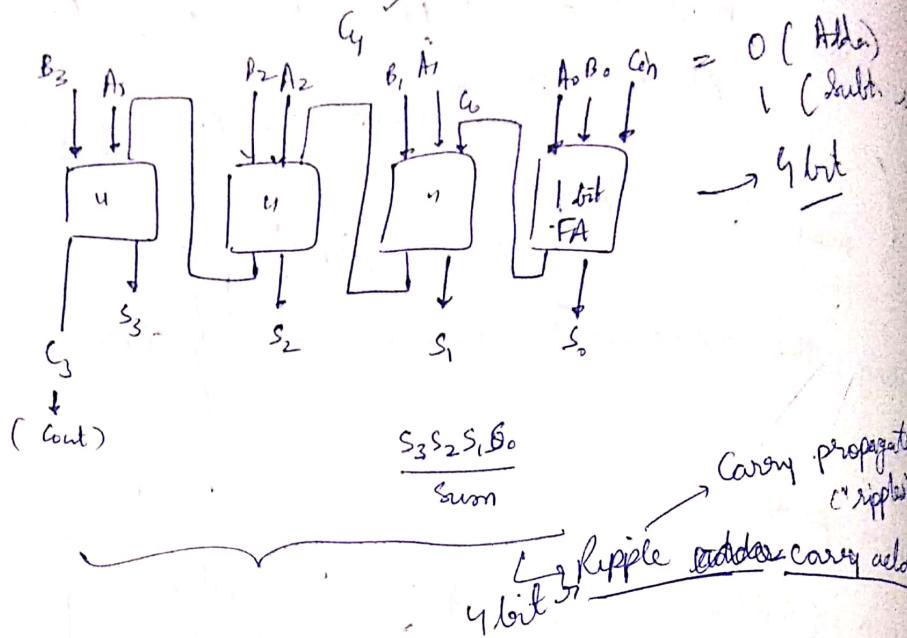
$$\begin{array}{r}
 C_3 \quad C_2 \quad C_1 \quad C_0 \\
 \text{---} \\
 A_4 \quad A_3 \quad A_2 \quad A_1 \quad A_0 \\
 B_4 \quad B_3 \quad B_2 \quad B_1 \quad B_0 \\
 \hline
 S_4 \quad S_3 \quad S_2 \quad S_1 \quad S_0
 \end{array}$$



Time required ? =

$t_{add}$  → Addition time



$t$  → Time to generate the carry

$t_{prop}$  → Carry propagation time

$$t = 4 \cdot t_{add} + (4-1) t_{prop}$$

$\underbrace{(n-1)}_{\text{in}} \underbrace{\text{dominates}}$

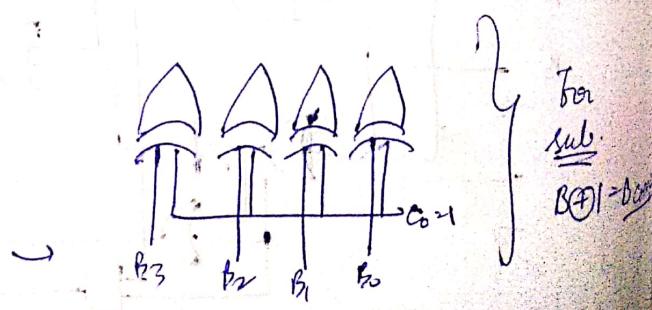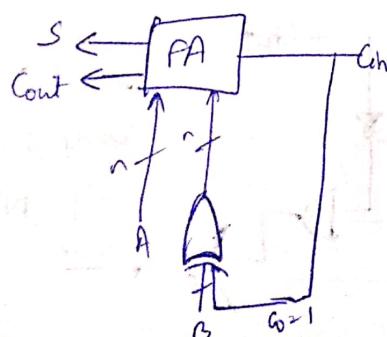∴  $n$ -bit ripple carry:  $n t_{add} + (n-1) t_{prop}$   
 $\underbrace{\qquad\qquad\qquad}_{\text{Sort of } \underline{(dn)} \text{ time}}$



\* fast adder

\* carry loop ahead adder

### CLA Adder:

$$C_{out} = AB + BC + CA$$

Carry generate:  $A \cdot B$  ( $g_i$ )

Carry propagate:  $A + B$  ( $p_i$ ) (can be XOR also)

$$G_i = A_i \cdot B_i + G_{i-1} (A_i + B_i)$$

$$G_i = g_i + p_i G_{i-1}$$

$$C_0 = A_0 B_0 + G_0 (A_0 + B_0) = g_0 + p_0 G_0$$

$$G_1 = g_1 + p_1 G_0$$

$$= g_1 + p_1 (g_0 + p_0 G_0)$$


$$= g_1 + p_1 g_0 + p_1 p_0 G_0$$

$$C_1 = g_2 + p_2 G_1$$

$$= g_2 + p_2 g_1 + p_1 p_2 g_0 + p_2 p_1 p_0 G_0$$


$$C_2 = g_3 + p_3 G_2$$
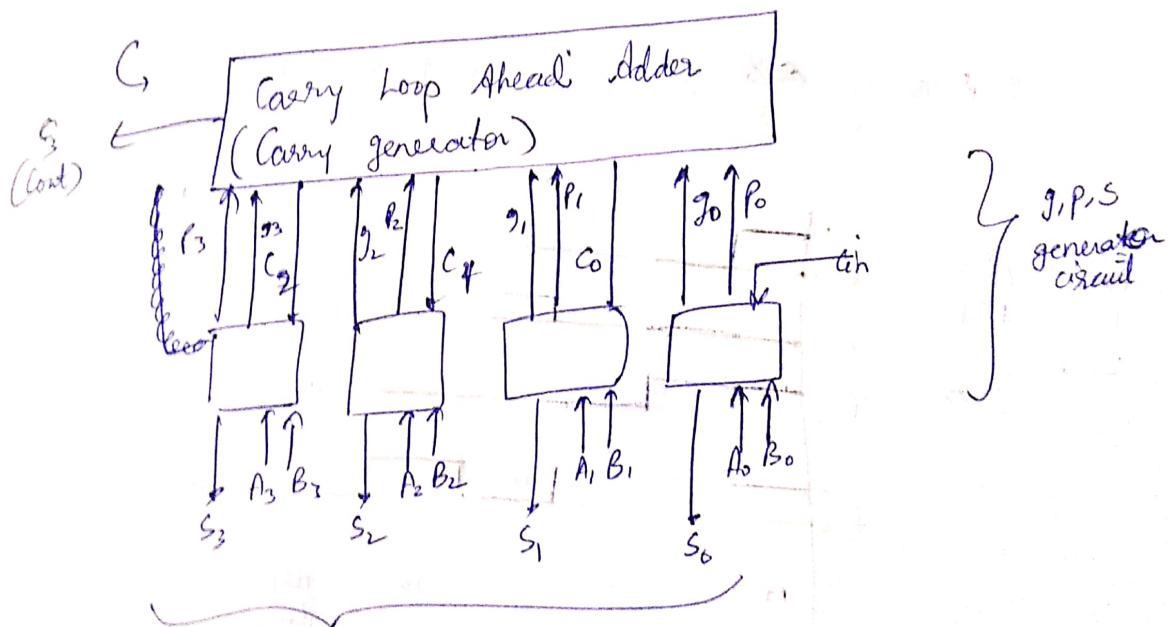
$$= g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 G_0$$



Parallelly all process occurs.  
pure combinational & OR circuit  
V. fast.
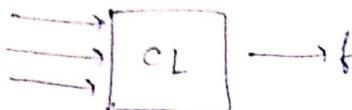
## # Hazards in Combinational circuits :-



Change in the input


$$\begin{array}{ll} I_a \rightarrow I_a' & f = 1 \rightarrow 0 \\ I_b \rightarrow I_b' & f = 0 \rightarrow 1 \end{array}$$

$I_1 \rightarrow I_1'$        $f = 1$   
 $I_2 \rightarrow I_2'$        $f = 1$


Static - 1 hazard

$$\begin{array}{ll} I_3 \rightarrow I_3' & f = 0 \\ I_4 \rightarrow I_4' & f = 0 \end{array}$$

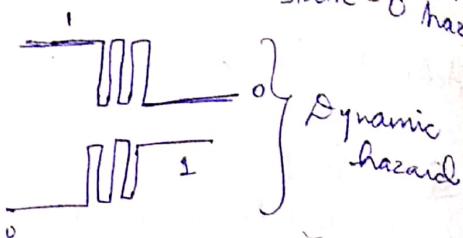$I_3 \rightarrow I_4'$   
 Static - 0 hazard




→ Happens due to differences of delay

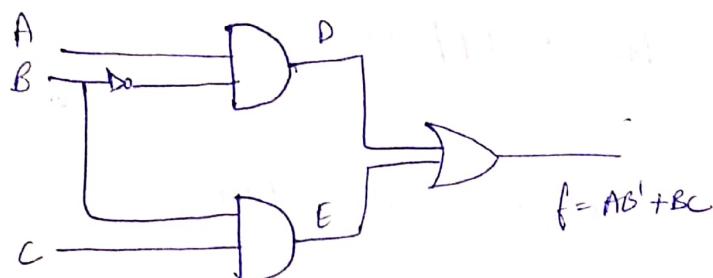

→ Delay of each gate is 10 ns. (say)
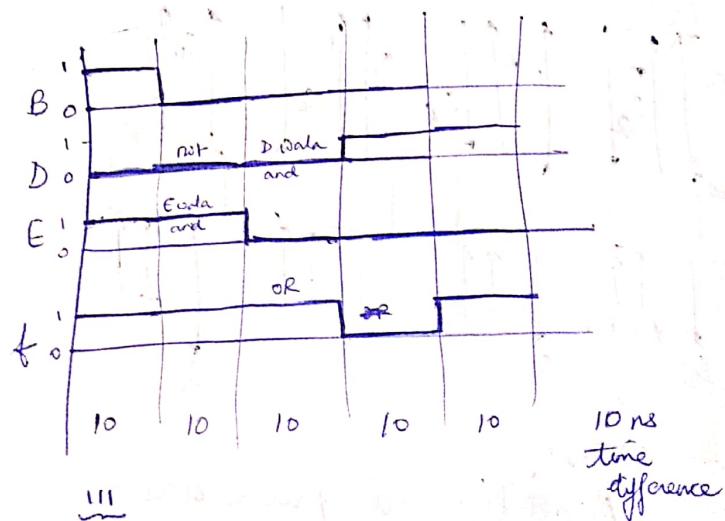
$$\begin{array}{l} ABC \rightarrow ABC \\ \text{---} \quad \text{---} \\ 111 \quad 101 \end{array}$$



K-map

	BC	AB	CD	00	01	11	10
A	0	0	0	0	0	1	1
B	0	0	1	0	1	0	1
C	1	1	0	0	1	0	0

DOBT

Hazard or  
not hazard

$$AB + BC \Rightarrow (AC)$$

$$\dots (AB) \rightarrow \text{hazard}$$



Find Adjacent 1's which  
are not covered


by the same term.

For that one, we will have hazard  
To make it we lets

### # Product of sum comparison

$$f = (A+C)(A'+D')(B'+C'+D)$$


	CD	00	01	11	10
AB	0	0	0	0	0
00	0	0	0	0	0
01	0	0	1	0	0
11	0	0	0	0	0
10	0	0	0	0	0

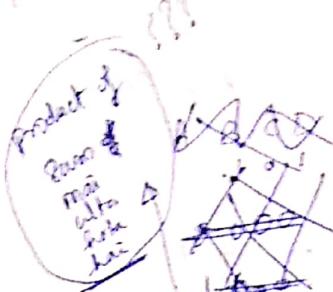

$$\left[ \begin{array}{l} A'B'C'D = 1111 \\ A'B'C'D = 1110 \end{array} \right] \text{ Hazard}$$

Such terms add karna padegenge to eliminate hazard
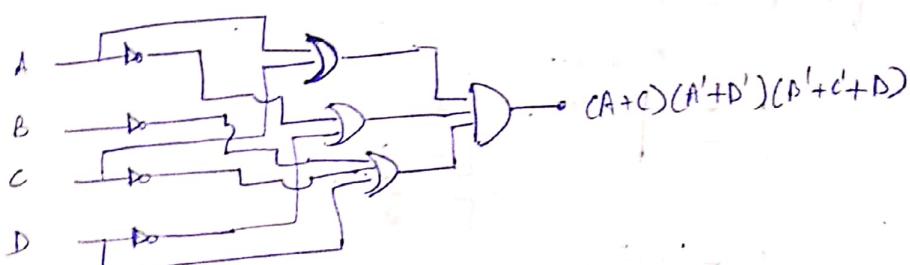
$$f = (A+C)(A'+D')(B'+C'+D)(C+D) \underbrace{(A+B'+D)}_{\text{ye add kara to avoid hazards}} (A'+B'+C')$$



It is simple and the time taken for the output is less  
but still there is a hazard again for the output

So we can add some extra terms to avoid the hazard

Method 1: Add  $(A+B'+D)$  and  $(A'+B'+C')$

Method 2: Add  $(A+B'+D)$  and  $(A'+B'+C')$

## # Realizing combinational circuits with NAND/NOR logic

1) Two level ckt



$$f = A + BC' + B'CD \rightarrow \text{SOP} - \underline{\text{AND-OR ckt}}$$

$$f = (f')' = ((A + BC' + B'CD)')' = (\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D})' \\ = (A') \cdot (BC')' \cdot (B'CD)'$$

$\hookrightarrow \underline{\text{NAND-NAND}}$

$$f = (A' \cdot (B'C) \cdot (B + C'D'))' \rightarrow \underline{\text{OR-NAND}}$$

$$f = (A + BC' + B'CD)$$


$$= (A')' + (BC')' + (B'CD)'$$

$$= (A')' + (B'C)' + (B + C'D')'$$

$\hookrightarrow \underline{\text{NOR-OR}}$

# How to →

$$f = A + BC' + B'CD$$

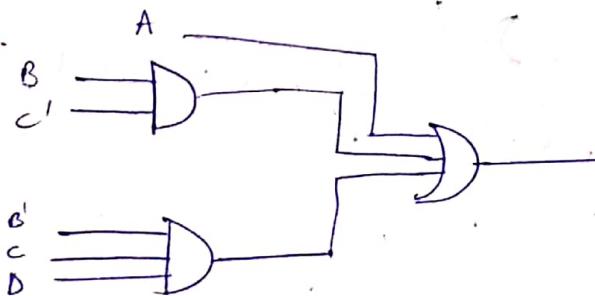

SOP

→ Replace all gates by NAND gates.

→ If any single literal exists at the input of the last OR, then complement the literal.


??

(Kya tha)

$$F_{\text{SOP}} = l_1 + l_2 + \dots + l_m + p_1 + p_2 + \dots + p_n$$

$l_1, l_2, \dots, l_n \rightarrow$  single literals

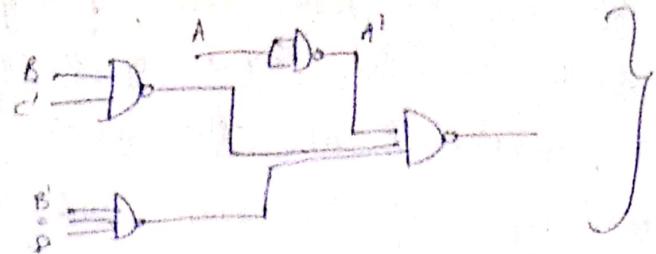$p_1, p_2, \dots, p_n \rightarrow$  product terms



Two level  
realisation  
also known as  
fan-in & fan-out

[ fan-in &  
fan-out  
by a pair ]

### # Multi-level realisation with NAND-NOR


$$F = a' [ b' + c(d+e') + fg' ] + hi'j + k$$

→ Realize AND-OR ckts (SOP)


→ Realize the ckt with  $x$ -input AND-OR ( $1 \leq x \leq 4$ )

Realization:

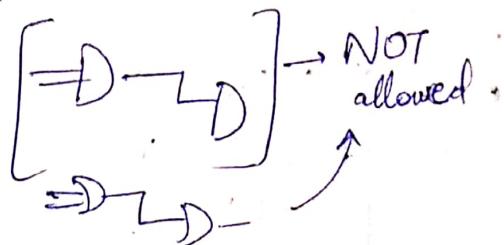$\checkmark$  [ output of AND (OR) gate cannot be fed to the input of AND (OR) gate. ]




AO type circuit -

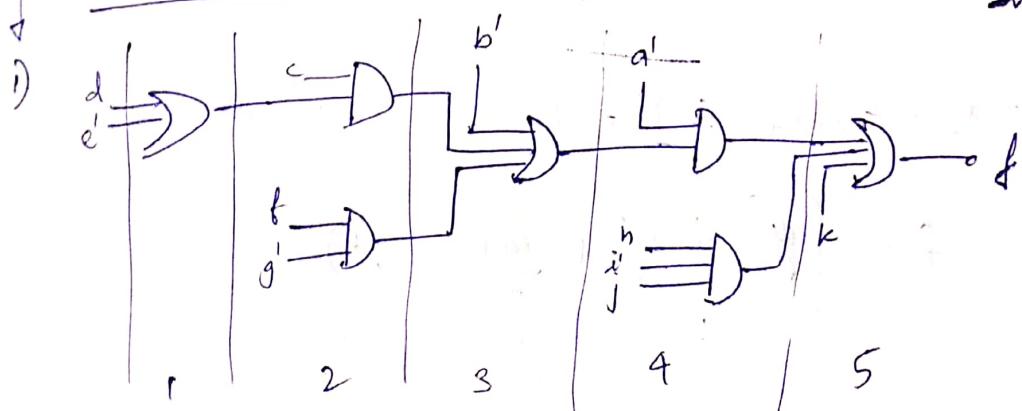


→ OA type?

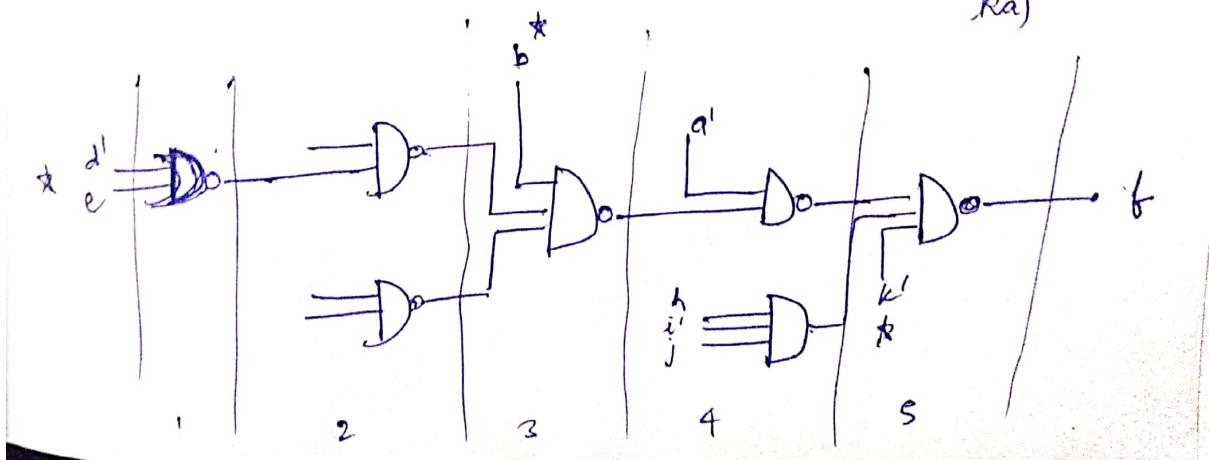2) Replace gates by NAND gate, & w/o complemented input dena  
OR pe. (individual literals  
ka)



→ After replacing all gates by NAND gates, if any single literal exists at the input of the odd level gates (OR), complement all the single literals. Don't change the input of the even level gates.
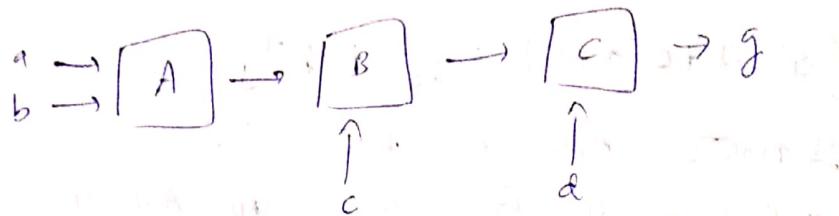
$$g(x_1, x_2, x_3, x_4) = \sum(4, 6, 7, 15) + \cancel{\sum}(2, 3, 5, 11)$$



Find the minterms b/w  $x_1, x_2, x_3, x_4$  & determine  $A, B, C$

$x_1, x_2$	00	01	11	10
$x_3, x_4$	00	01	11	10
$x_1$	0	1	1	1
$x_2$	0	0	1	0
$f(x)$	0	1	1	0

$4 \times 4 \rightarrow 2^4 = 16$  possible fns

$(x_1 x_2 + x_3 x_4) \Rightarrow \underline{\text{Min fns}}$  → isme is form may nahi aa sakte

for  $f = f_3(f_2(f_1(a, b), c), d)$

$\underbrace{f_1}_{A} (a, b)$        $\underbrace{f_2}_{B} (f_1(a, b), c)$        $\underbrace{f_3}_{C} (f_2(f_1(a, b), c), d)$

